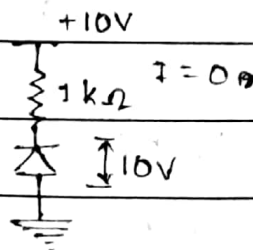
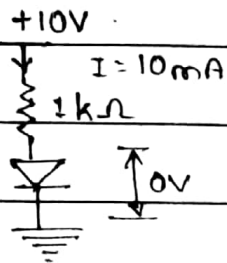


unit-01

chap-01 : Diode modeling and applications.

$$V = IR$$

Ideal diode : Forward bias - short circuit

Reverse bias - open circuit

$$I_D = I_S e^{\left(\frac{V_D}{nV_T}\right)} \quad \text{--- (A)}$$

 $I_D$  = diode current $V_D$  = diode voltage $n$  = 1 or 2 $V_T$  = Thermal voltage = 25mV at room temp.

$$V_T = \frac{kT}{q}$$

 $I_S$  : Saturation or Scaling current (order of  $10^{-15}$  A)

Let us assume that a diode carries carrier current  $I_{D1}$  when its voltage is  $V_{D1}$  under forward bias conditions. Let us say changed current of  $I_{D2}$  thro. that diode when its volt is  $V_{D2}$ . Let us use eqn 'A' for this connection.

$$I_{D1} = I_S \cdot e^{V_{D1}/n \cdot V_T} \quad \text{--- (1)}$$

lly.

$$I_{D2} = I_S \cdot e^{V_{D2}/n \cdot V_T} \quad \text{--- (2)}$$

$$\textcircled{2} \div \textcircled{1}$$

$$\frac{I_{D2}}{I_{D1}} = \frac{I_S \cdot e^{V_{D2}/n \cdot V_T}}{I_S \cdot e^{V_{D1}/n \cdot V_T}} \quad \text{--- (3)}$$

$$\ln \frac{I_{D2}}{I_{D1}} = \frac{V_{D2} - V_{D1}}{n \cdot V_T} \quad \text{--- (4)}$$

$$V_{D2} - V_{D1} = n \cdot V_T \ln \frac{I_{D2}}{I_{D1}} \quad \text{--- (5)}$$

$$V_{D2} - V_{D1} = 2.3 n \cdot V_T \log_{10} \frac{I_{D2}}{I_{D1}} \text{ volts} \quad \text{--- (6)}$$

when there is decade change in the current for ex. when  $I_{D1} = 1\text{mA}$  then  $I_{D2} = 10\text{mA}$ . Substituting this in above eqn. we have change in diode voltage.

$$V_{D2} - V_{D1} = 2.3 n \cdot V_T \cdot 1$$

$$\Delta V_D = V_{D2} - V_{D1} = 2.3 n \cdot V_T \quad \text{--- (7)}$$

eqn (7) shows change in diode voltage when there is decade change in the current.

While designing diode ~~seffer~~ ~~sobber~~ this term will be given as one of its specification of the diode.


10/08/2019

## Diode Models:

1. An exponential model  $\rightarrow$  Graphical method  
 $\rightarrow$  Iterative method.
2. Piece-wise linear model.
3. constant voltage drop or 0.7V drop model.
4. An ideal diode model.
5. Small-signal model.

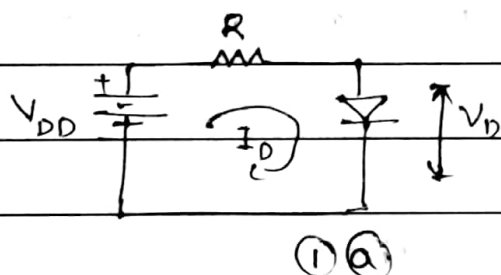1. Exponential model. (Accurate model).

$$I_D = I_S e^{V_D / n V_T} \quad \text{--- (1)}$$



$$V_{DD} = I_D R + V_D \quad \text{--- (2)}$$

$$I_D = \frac{V_{DD} - V_D}{R} \quad \text{--- (3)}$$

a) Graphical method

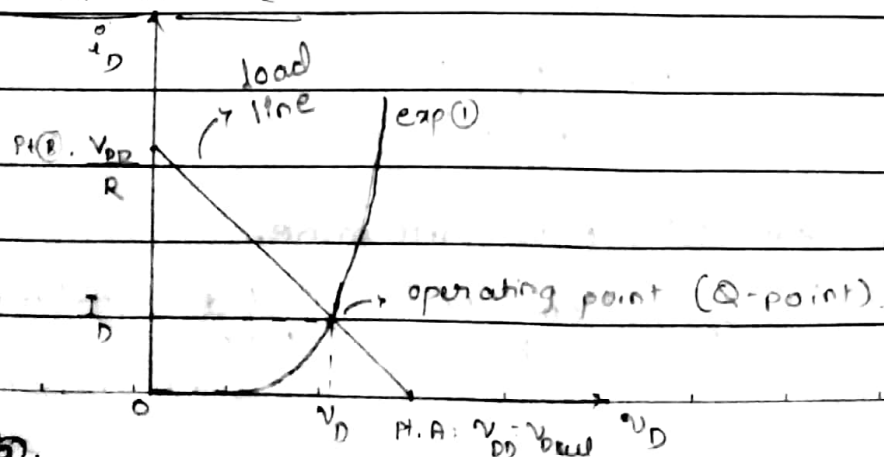


Fig 1a

consider eqn (3)

$$\text{Let, } I_D = 0.$$

$$V_D = V_{D_{cut}} \longrightarrow \text{pt (A)}$$

$$\text{let } V_D = 0.$$

$$I_{D_{sat}} = \frac{V_{DD}}{R} \longrightarrow \text{pt (B)}$$

DC load line.

b) Iterative method:

for complex circuit graphical method of determining  $V_D$  &  $I_D$  will be tedious & hence this graphical method is used only for simple circuit.

b) Iterative method:

Ex : 1) Determine the current  $I_D$  & the diode volt.  $V_D$  for the circuit shown in fig 1A. when  $V_{DD} = 5V$  &  $R = 1k\Omega$ , assume that diode has the current of  $1mA$ . At a voltage of  $0.7V$ . and its volt. drop changes by  $0.1V$  for every decade change in current

Sol<sup>n</sup>:

$$V_{DD} = 5V, \quad R = 1k\Omega, \quad V_{D_1} = 0.7V, \quad I_{D_1} = 1mA.$$

$$V_D = ?, \quad I_D = ?$$

using eqn (3) let us determine.

$$I_{D_2} = \frac{V_{DD} - V_{D_1}}{R} = \frac{5 - 0.7}{1000} = 4.3mA.$$



wkt.

$$(2.3nV_T = 0.1V/\text{decade})$$

$$V_{D2} - V_{D1} = 2.3nV_T \log \frac{I_{D2}}{I_{D1}}$$

$$V_{D2} = 0.7 + 0.1 \times \log \frac{4.3 \text{ mA}}{1 \text{ mA}}$$

$$= 0.7 + 0.063$$

$$\therefore V_{D2} = 0.763 \text{ V}$$

Note: (\*) Comparing  $I_{D1}$  &  $I_{D2}$  values. as a diff. is more one more iteration is req.

2nd iteration:  $I_{D2}' = \frac{V_{DD} - V_{D2}}{R}$

$$= \frac{5 - 0.763}{1000} = 4.237 \text{ mA}$$

$$V_{D2}' - V_{D2} = 0.1 \times \log \frac{I_{D2}'}{I_{D2}}$$

$$\therefore V_{D2}' = V_{D2} + 2.3nV_T \log \frac{I_{D2}'}{I_{D2}}$$

$$V_{D2}' = 0.763 + 0.1 \times \log \left( \frac{4.237}{4.3} \right)$$

$$V_{D2}' = 0.762 \text{ V}$$

(\*) comparing the values of  $I_D$  &  $V_D$  of 1st & 2nd iteration. we can say that diff. is less hence. we can.

consider the results of 2<sup>nd</sup> iteration as final values of  $I_D$  &  $V_D$  for the circuit shown

$$\therefore \begin{cases} V_D = 0.762 \text{ V} \\ I_D = 4.237 \text{ mA} \end{cases}$$

\* This iterative method of determining ideal  $V_D$  will be tedious one when no. of iterations are more naturally for complex circuit no. of iteration will increase & hence this method is useful only for simple circuits where no. of iterations are less and we can get accurate values of  $V_D$  &  $I_D$ .

## 2. Piece-wise linear model:


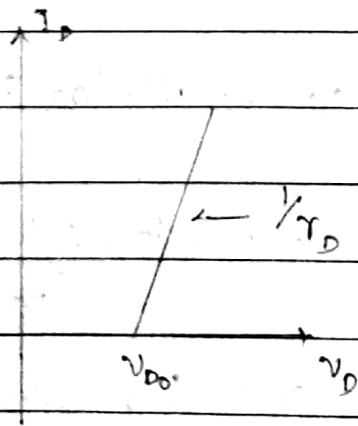


fig 2 @ V-I characteristics


\* where  $V_{D0} = V_r$  = cut-in voltage of the diode.

$r_D$  = forward resistance.

fig 2(b) piece-wise linear model.

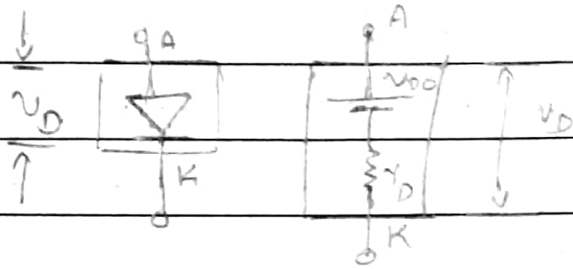

considering the circuit of fig 2(a)

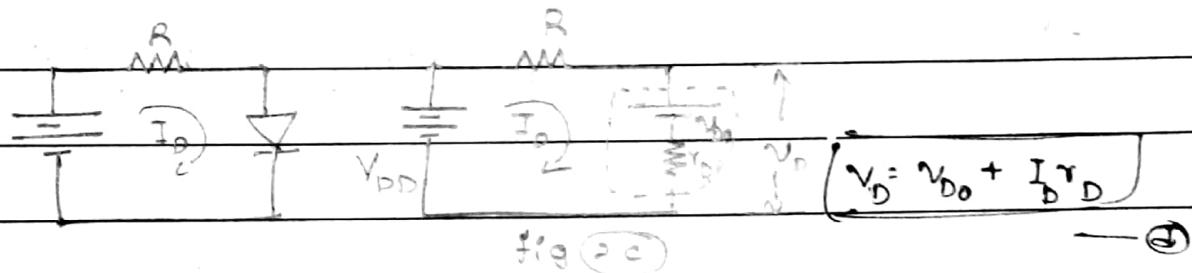

Applying KVL to fig 2(c)

$$V_{DD} = I_D R + V_{D0} + I_D r_D \quad \text{--- (a)}$$

$$V_{DD} = I_D (R + r_D) + V_{D0} \quad \text{--- (b)}$$

$$I_D = \frac{V_{DD} - V_{D0}}{(R + r_D)} \quad \text{--- (c)}$$

Ex. considering the ex. taken in the previous model let us determine ideal \$V\_D\$ values when piece-wise linear model. parameters are given as. \$V\_{D0} = 0.65\$ V, \$r\_D = 20\$ \$\Omega\$.

Soln: 
$$I_D = \frac{5 - 0.65}{1000 + 20}$$

$$I_D = 4.26 \text{ mA.}$$

$$V_D = V_{D0} + I_D r_D$$

$$= 0.65 + (4.26 \times 10^{-3})(20) = 0.735 \text{ V}$$

11/08/2017

\*. comparing  $I_D$  &  $V_D$  values of piece-wise linear model with iterative analysis. we can say that diff. is less and result of the approx. analysis which is piece wise linear model analysis is better comparing with the iterative analysis.

③ Constant voltage drop volt. model or 0.7V model.



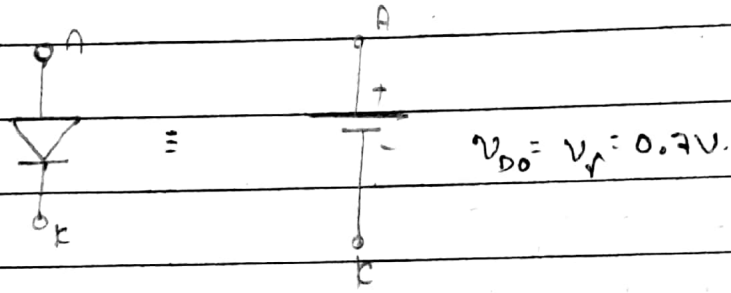


Fig ③ ① . .

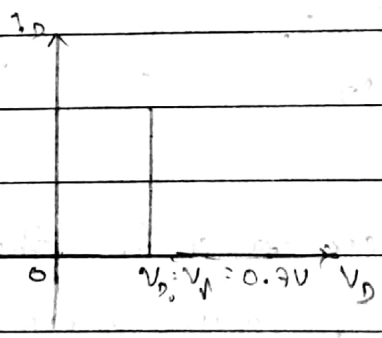

③ ② vi. chan.

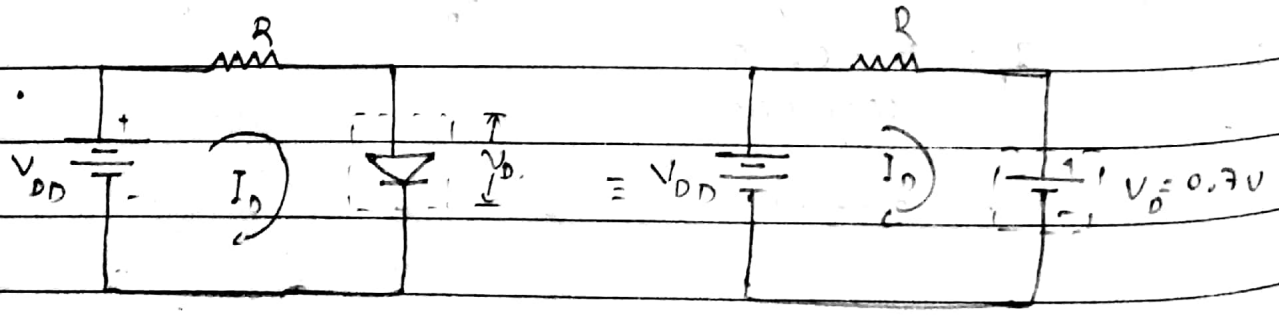

$$* I_D = \frac{V_{DD} - V_D}{R}$$

consider, same ex. which has taken from the 1<sup>st</sup> model but it should be noted that under specification of const. volt of 0.7V has to be given then itself will be diode volt.  $V_D$  and corresponding current can be determined using eqn.

$$I_D = \frac{V_{DD} - V_D}{R}$$

Hence, diode volt. and diode current are.

$$V_D = 0.7V \text{ (const).}$$

$$I_D = 4.3mA.$$

$$V_{D0} = 0.7V = V_D.$$

$$I_D = \frac{V_{DD} - V_{D0}}{R} = \frac{5 - 0.7}{1000} = 4.3mA.$$

\* comparing these results in the previous models we can say that these are not ~~too~~<sup>too</sup> diff. from the values obtained from previous models.

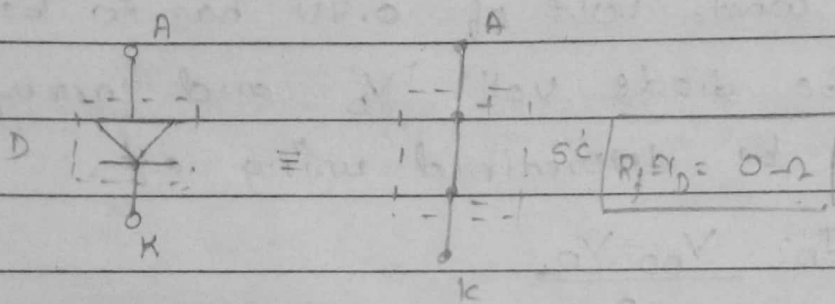
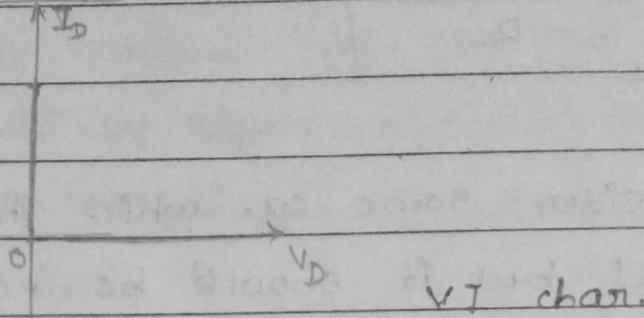
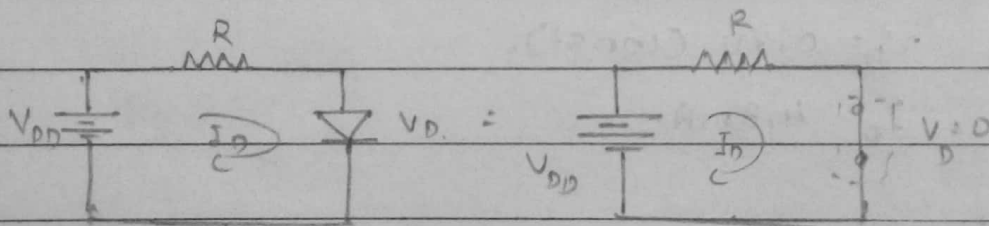
4. Ideal diode model.

Fig 4(a)



$$I_D = \frac{V_{DD} - V_D}{R} = \frac{5}{1k} = 5mA$$

$$\text{here } V_D = 0V$$

Problems.


- For from the follo. circuit determine the values of  $I_D$  &  $V_D$  when  $V_{DD} = 5V$ , and  $R = 10k\Omega$  assume that diode has the voltage of  $0.7V$  at  $1mA$  current. and the voltage changes by  $0.1V/\text{decade}$  current change

use (a) Integration method.

(b) Piece-wise linear model with  $V_{D0} = 0.65 \text{ V}$

B.Y.D = 20-2.

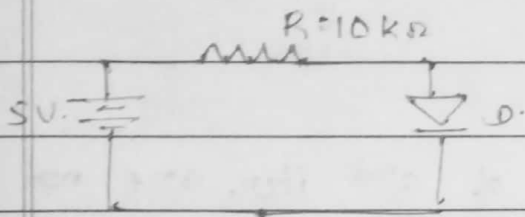(c) const. volt. drop model with  $V_D = 0.7 \text{ V}$ .



sol<sup>n</sup>: (a) Iterative method.:

$$V_{D1} = 0.7 \text{ V}, \quad I_{D1} = 1 \text{ mA}.$$

1<sup>st</sup> iteration

$$I_{D2} = \frac{V_D - V_{D1}}{R} = \frac{5 - 0.7}{10 \text{ k}\Omega} = 0.43 \text{ mA}.$$

$$V_{D2} - V_{D1} = 2.3 \text{ nV} \log \frac{I_{D2}}{I_{D1}}$$

$$V_{D2} - 0.7 = (0.1) \log \left( \frac{0.43 \times 10^{-3}}{1 \times 10^{-3}} \right)$$

$$V_{D2} = 0.6633 \text{ V}.$$

as an instant values. of  $I_{D2}$  &  $V_{D2}$  are much diff. from the values of  $I_{D1}$  &  $V_{D1}$ . Hence 2<sup>nd</sup> iteration is required.

2<sup>nd</sup> iteration:

$$I_{D2}' = \frac{V_{DD} - V_{D2}}{R} = \frac{5 - 0.6633}{10000} = 0.4337 \text{ mA}.$$



$$V_{D2}' = V_{D2}^0 + 2.3nV_T \log \left( \frac{I_{D2}'}{I_{D2}} \right)$$

$$= 0.6633 + (0.1) \log$$


$$V_{D2}' = 0.6636 \text{ V}$$

as values of  $I_{D2}$  &  $V_{D2}$  of 2<sup>nd</sup> iter. are not much diff from the values obtained from 1<sup>st</sup> iteration we can consider  $V_{D2}'$  &  $I_{D2}'$  as the final values of diode volt. & current.

$$\text{ii } \begin{cases} V_D = 0.6636 \text{ V} \\ I_D = 0.4332 \text{ mA} \end{cases}$$

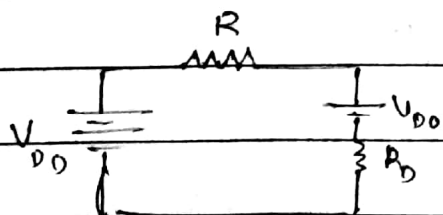(b) piece-wise.

$$V_{DD} = 0.65 \text{ V}, \quad R_D = 20 \text{ } \Omega$$



$$I_D = \frac{V_{DD} - V_{D0}}{R + R_D}$$

$$= \frac{5 - 0.65}{10 \text{ k}\Omega + 20}$$

$$= 0.434 \text{ mA}$$




$$V_D = V_{D0} + I_D R_D$$

$$= 0.65 + (0.434 \times 10^{-3})(20)$$

$$V_D = 0.6587 \text{ V}$$

©

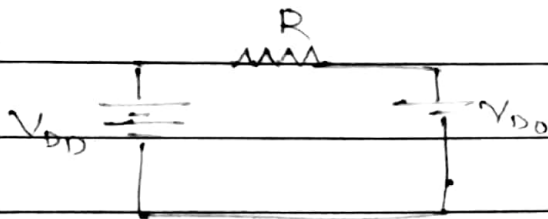

$$V_{D0} = 0.7 \text{ V}$$

$$V_D: I_D = \frac{V_{DD} - V_{D0}}{R} = \frac{5 - 0.7}{10 \text{ k}\Omega}$$


$$= 0.43 \text{ mA}$$

$$V_D = 0.7 + (0.43 \times 10^{-3})$$

$$V_D = 0.7 \text{ V}$$

②

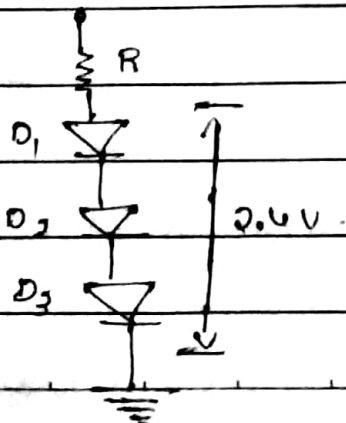Design the follo. circuit to provide an o/p volt. of 2.4 V. assume that the diodes available have 0.7 V drop at 1 mA current and  $\Delta V = 0.1 \text{ V}$  / decade current change.



Sol<sup>n</sup>.  $V_{D1} = 0.7V$ ,  $I_{D1} = 1mA$   $\Delta V = 2.3nV_T = 0.1$

$$V_{D2} = \frac{V_0}{3} = \frac{2.4}{3} = 0.8V$$

$$V_{D2} - V_{D1} = 2.3nV_T \log \frac{I_{D2}}{I_{D1}}$$

$$(0.8 - 0.7) = 0.1 \log \frac{I_{D2}}{I_{D1}}$$

$$10 = 0.1 \log \frac{I_{D2}}{I_{D1}}$$

$$10 = \frac{I_{D2}}{1mA}$$


$$I_{D2} = 10mA$$

Let  $V_R$  be the volt. across the resistor.

$$V_R = 10 - V_0 = 10 - 2.4 \\ = 7.6V //$$

$$R = \frac{V_R}{I_{D2}} = \frac{7.6}{10mA} = 760\Omega \text{ or } \underline{0.76k\Omega}$$

3)

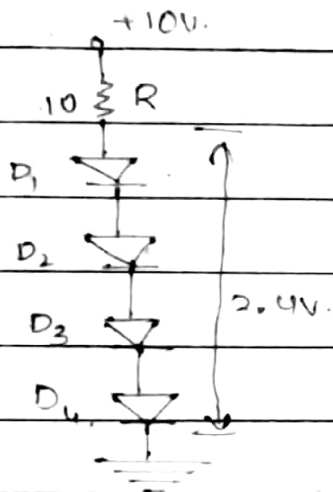Sol<sup>n</sup>.

$$V_{D1} = 0.7V, \quad I_{D1} = 1mA, \quad \Delta V_D = 2.3nV_7 = 0.1$$

$$V_{D2} = V_D = \frac{2.4}{4} = 0.6V$$

$$V_{D2} - V_{D1} = 2.3nV_7 \log \frac{I_{D2}}{I_{D1}}$$

$$0.6 - 0.7 = 0.1 \log \frac{I_{D2}}{I_{D1}}$$

$$-1 = \log \frac{I_{D2}}{I_{D1}}$$

$$I_{D2} = 0.01 \times 0.1mA$$

$$V_R = 10 - V_D = 10 - 2.4$$

$$= 7.6V$$


$$R = \frac{V_R}{I_{D2}} = \frac{7.6}{0.1mA} = 76k\Omega$$

14/08/12

Date : / /

Page No.:

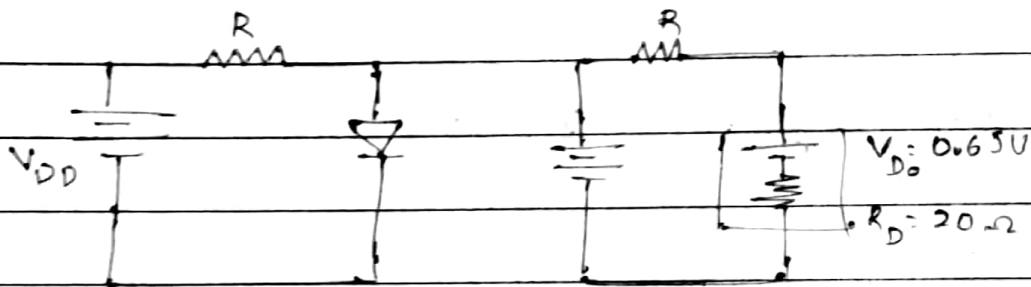- 1) consider the diode shown in follo fig. as junction area 100x larger than diode which are being used in the previous case where  $V_{D0} = 0.65V$  &  $R_D = 20\Omega$ . If we approx. characteristic, such a way that current is increasing 100x. then how are the model parameters  $V_{D0}$  &  $R_D$  will change.



Sol<sup>n</sup>:  $V_{D0} = 0.65V$ ,  $R_D = 20\Omega$ .

$$V = IR$$

$$V_{D0} = 0.65$$

$$R_D' = \frac{R_D}{100} = \frac{20}{100}$$

$$= 0.2\Omega$$

As per the data given increased jn. area of 2<sup>nd</sup> area will decrease it's resistance let us denote this resis. by  $R'$  and he said that VI chara. is in such a way that it's current carrying capacity is also increased by 100x hence as per this diagram. using ohm's law  $V = IR$ . cut-in volt.  $V_{D0}'$  will remain same as  $V_{D0}$  but


$$R_D' = \frac{R_D}{100} = \frac{20}{100} = 0.2\Omega$$

### 5) Small signal model of the diode:

when a diode is used in a circuit with the dc bias. along with an AC signal which has been super imposed on this dc then for this AC signal the eq<sup>u</sup> model of the diode. when signal variation is small, is called as small signal model of diode.

Before determining this small signal model the dc model, i.e. 0.7V model is used here for simplicity. The circuit dia. is shown in below fig (a) corresponding  $v_D$  charac. is also shown in below fig. along with small signal.

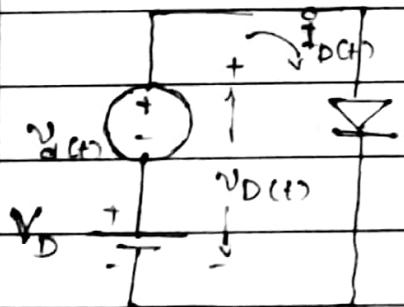For simplicity the series resistance 'R' is not considered in the below circuit.



$V_D$  - dc diode voltage

$v_d(t)$  - AC (inst) signal

$v_D(t)$  - total instantaneous

$$v_D(t) = V_D + v_d(t) \quad \text{--- (1)}$$

fig (a)

in the absence of instantaneous small signal  $v_d(t)$  i.e.  $v_d(t) = 0$ .


then volt.  $V_D$  appears across the diode and this will be the dc volt. of the diode.

$r_d$ : ac resis.

$r_D$ : DC resis.

Date: / /

Page No.:

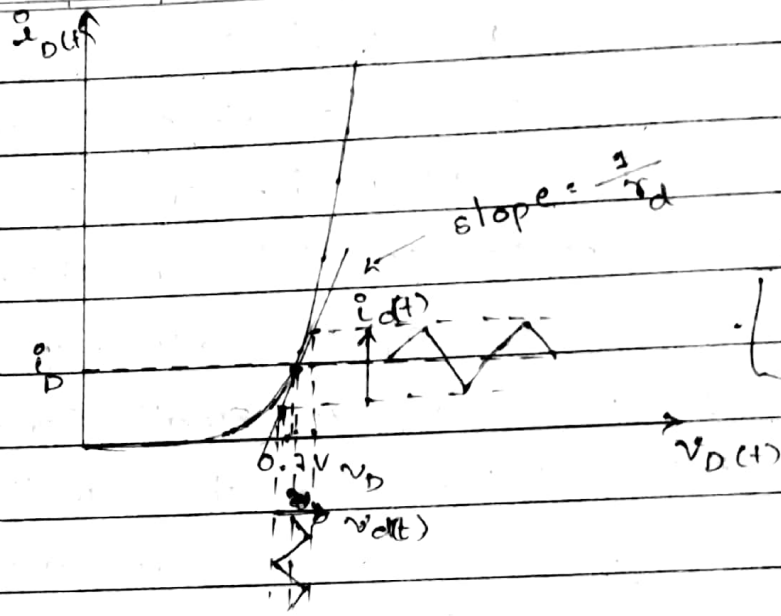

### Small signal analysis:

w.k.t

$$I_D = I_S e^{V_D / nV_T} \quad \text{--- (1)}$$

$V_D$  total inst. diode volt.

$$v_{D(t)} = V_D + v_d(t) \quad \text{--- (2)}$$

then,

total instantaneous diode current:

$$i_{D(t)} = I_S e^{v_{D(t)} / nV_T} \quad \text{--- (3)}$$

Substituting (2) in (3)

$$i_{D(t)} = I_S e^{(V_D + v_d(t)) / nV_T}$$

$$= I_S e^{V_D / nV_T} \times e^{v_d(t) / nV_T}$$

$$i_{D(t)} = I_D e^{v_d(t) / nV_T} \quad \text{--- (4)}$$

Let us consider the term  $e^{v_d(t) / nV_T}$ , expand it using Taylor's series.

Taylor's series:  $e^x = 1 + \frac{x}{1!} + \frac{x^2}{2!} + \dots$

Date: / /

Page No.:

$$e^{v_d(t)/nV_T} = 1 + \frac{v_d(t)/nV_T}{1!} + \frac{\{v_d(t)/nV_T\}^2}{2!} + \dots$$

In this case instantaneous signal  $v_d(t)$  is a small signal for ex. say  $v_d(t) = 0.01V$ . then in the Taylor's expansion when square of this term is taken its value will be negligible hence we neglect square term in this series so that.

$$e^{v_d(t)/nV_T} = 1 + \frac{v_d(t)}{nV_T} \quad \text{--- (6)}$$

Substituting (6) in (5) we get.

$$i_d(t) = I_D \left\{ 1 + \frac{v_d(t)}{nV_T} \right\} \quad \text{--- (7)}$$

$$i_d(t) = I_D + i_{d(t)} \quad \text{--- (8)}$$

considering  $i_{d(t)}$  term of eqn (7) & (8)

$$i_{d(t)} = \frac{I_D \cdot v_d(t)}{nV_T} \quad \text{--- (9)}$$

$$\therefore \frac{i_{d(t)}}{v_d(t)} = g_m = \text{small signal conductance of the diode} = \frac{I_D}{nV_T} \quad \text{--- (A)}$$

ly.


$$\frac{v_d(t)}{i_{d(t)}} = r_d = \text{small signal resistance of the diode} = \frac{nV_T}{I_D} \quad \text{--- (B)}$$

Note: 0

As seen. From eqn (B) from incrementing. resistance of diode  $\rightarrow$

$\rightarrow$  depends upon dc bias current of diode  $I_D$  along with values of  $n$  &  $V_T$ .

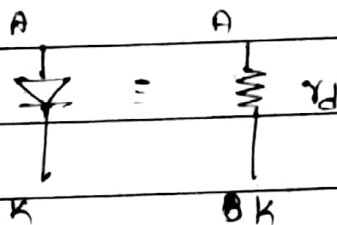1) The following fig give small signal model of diode



## Limiting circuits and clipping circuit

### Limiting circuits

1. Unbiased
2. biased.

### 1) Unbiased clipping circuit:

In these clipping circuits reference volt. which is denoted as  $V_R$  which is external dc source connected with the diode will be zero. and it is assumed that diode has  $0.7V$  cut in volt. with a forward resistance.  $R_f = r_D = 0$ , The following

&  $R_s = \infty$



for these unbiased clipping crts.

(i) Positive Clipping circuit.



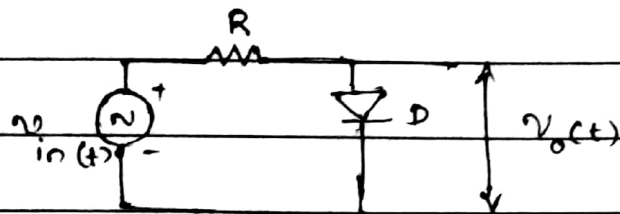


Fig. 1 (a)

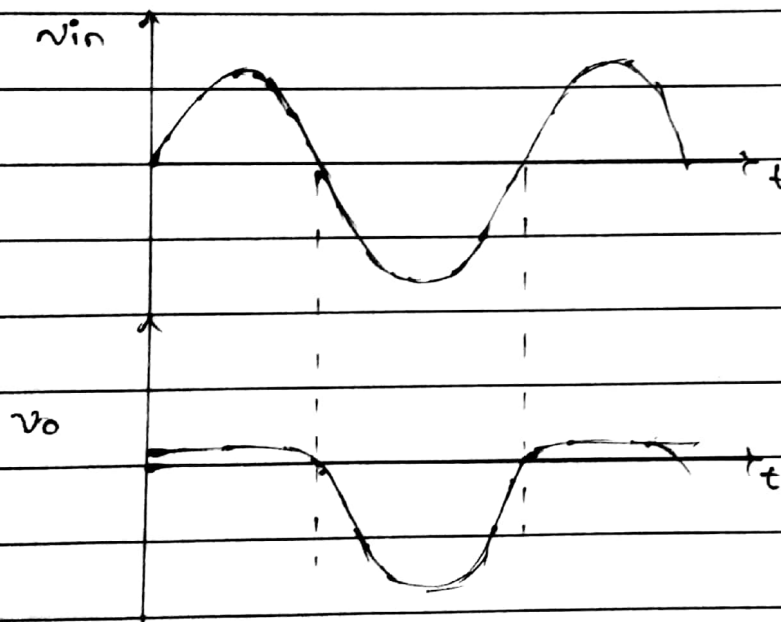

i/p & o/p  
waveforms.

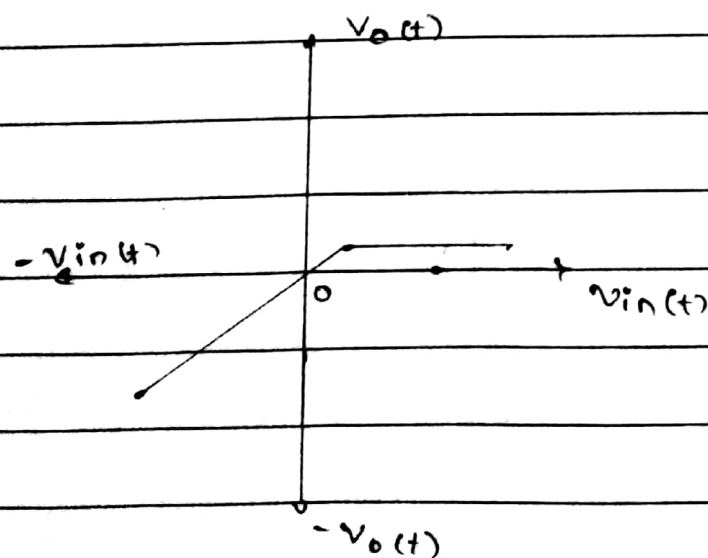

Transfer char. curve.

17/08/17

2) Negative clipping circuit.

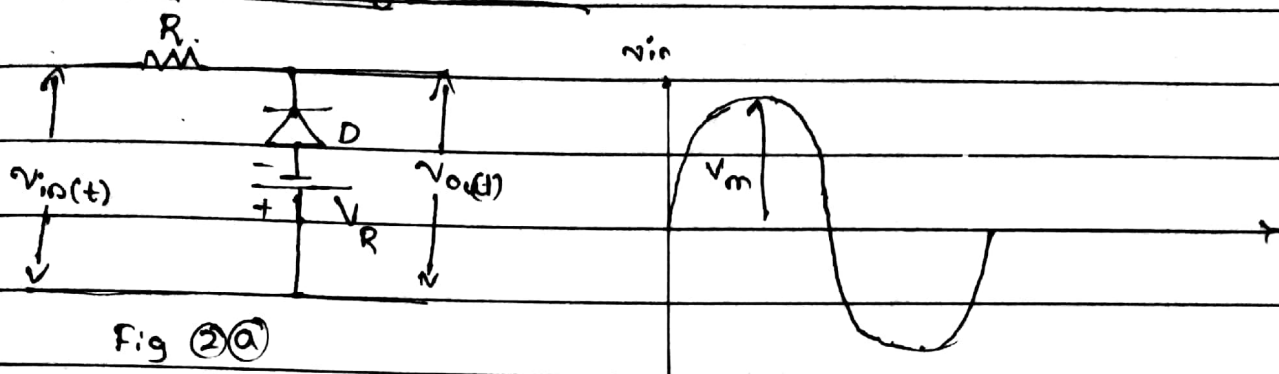


Fig 2(a)



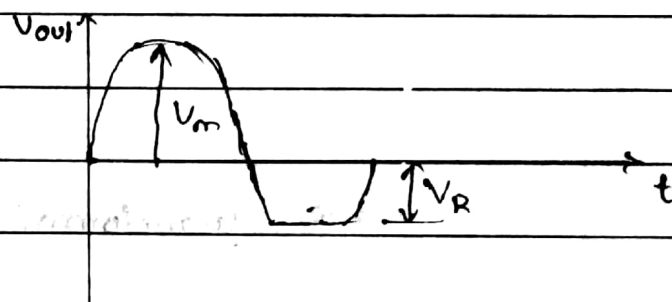


fig 2(b)


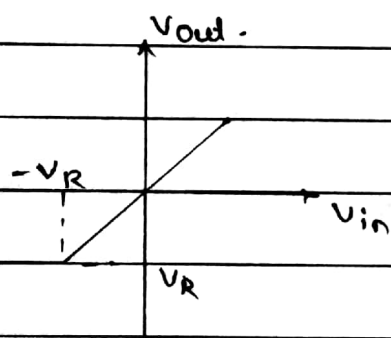


transfer characteristics.


3) Combination clipping.

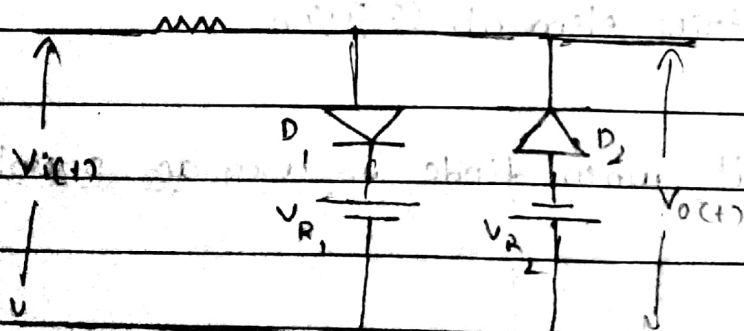

3a

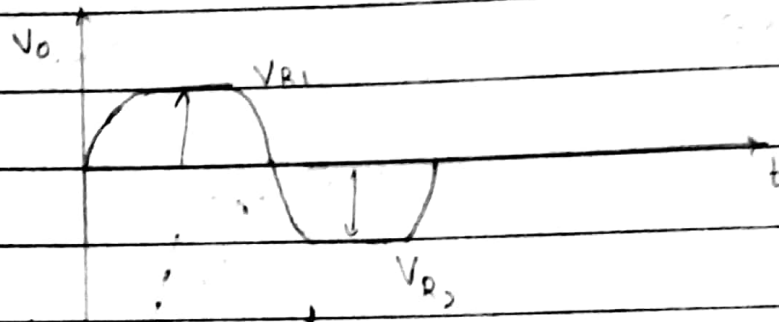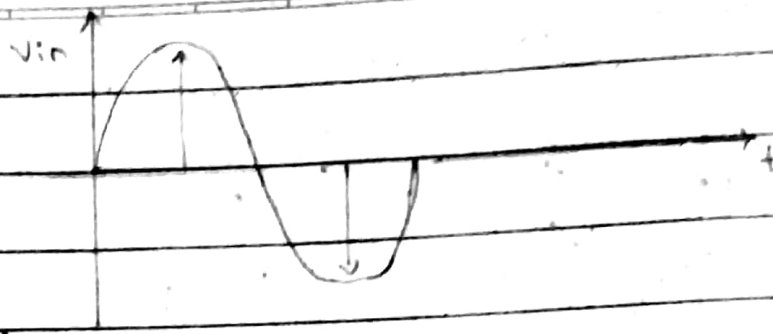


3.5 waveforms.


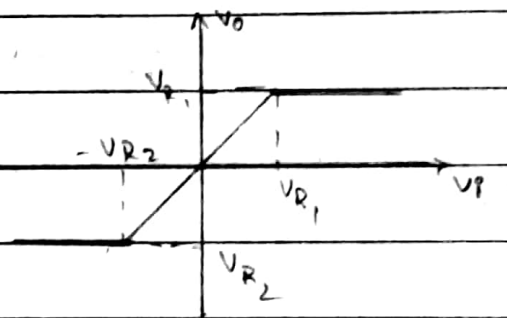


3c. transfer characteristics.

Clipping Circuits when diode is used as (a) shunt element and (b) a series element. (2 cr.)


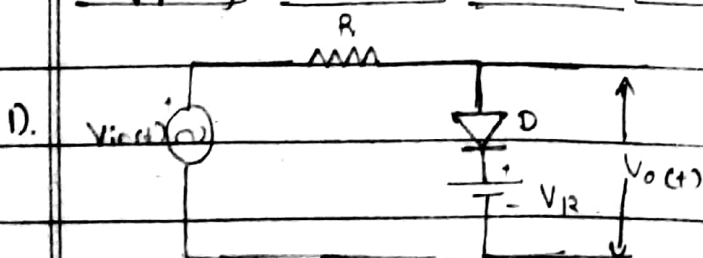
(a) Clipping circuit when diode is used as shunt element



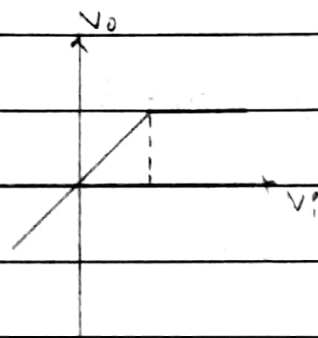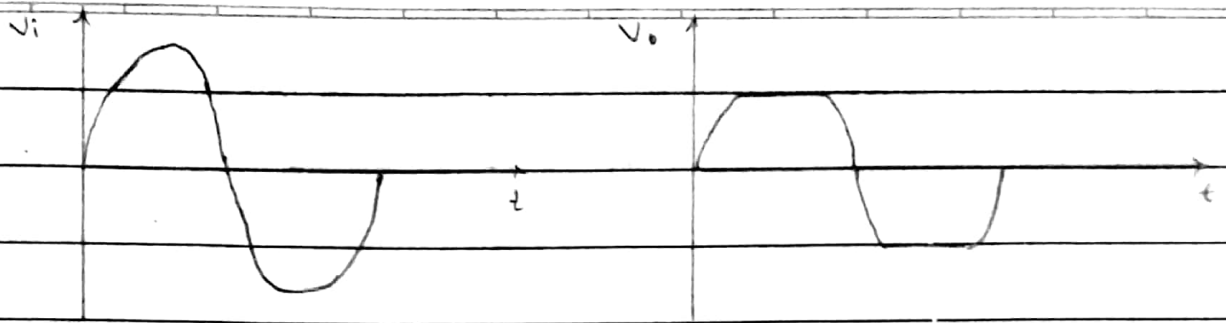

© transfer

2)

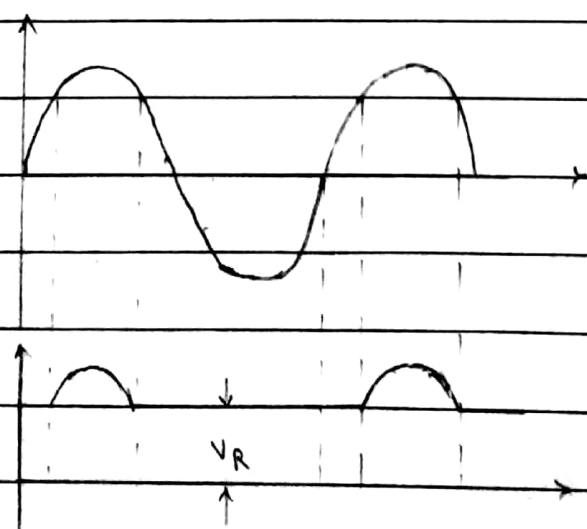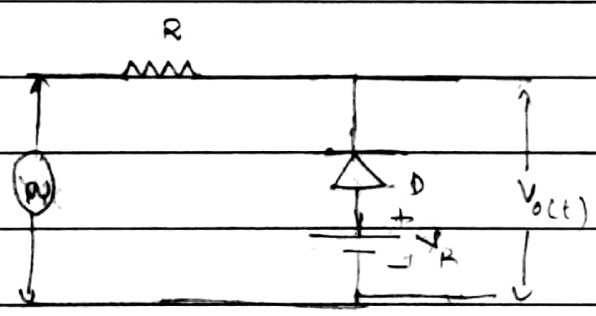

21/08/17

Q).



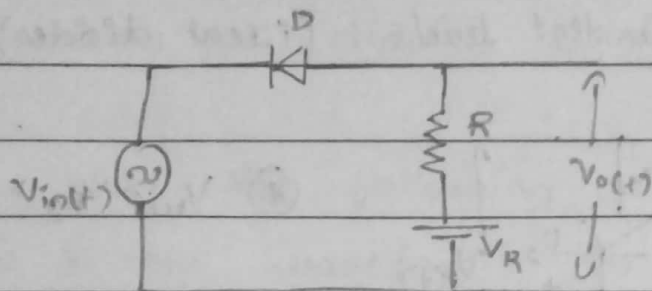
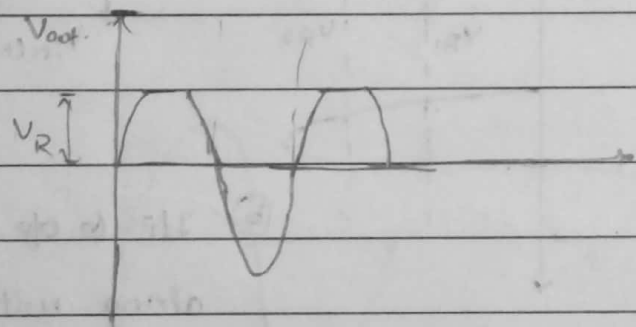


fig 2.a. Circuit diagram.

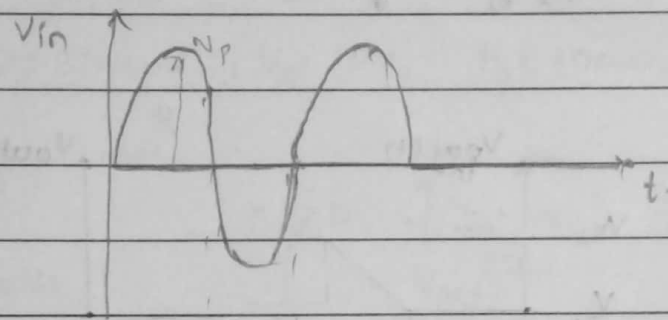


(b) waveforms

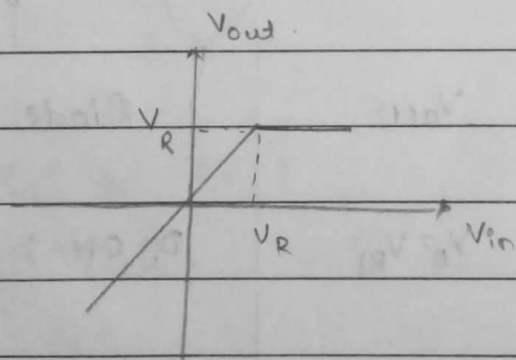

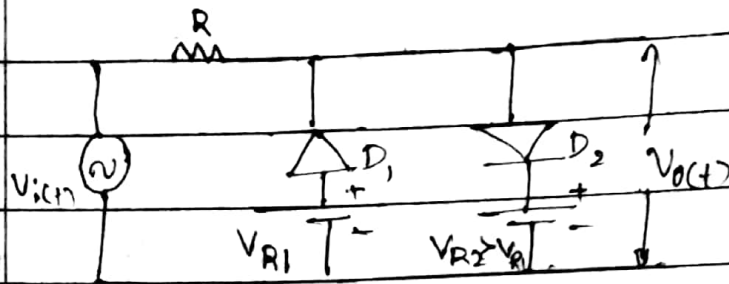(c) transfer char.


imp

Clipping at 2 independent levels. (ideal diodes)



$$* V_m > V_{R2} > V_{R1}$$

$$R = \sqrt{R_f \cdot R_r}$$

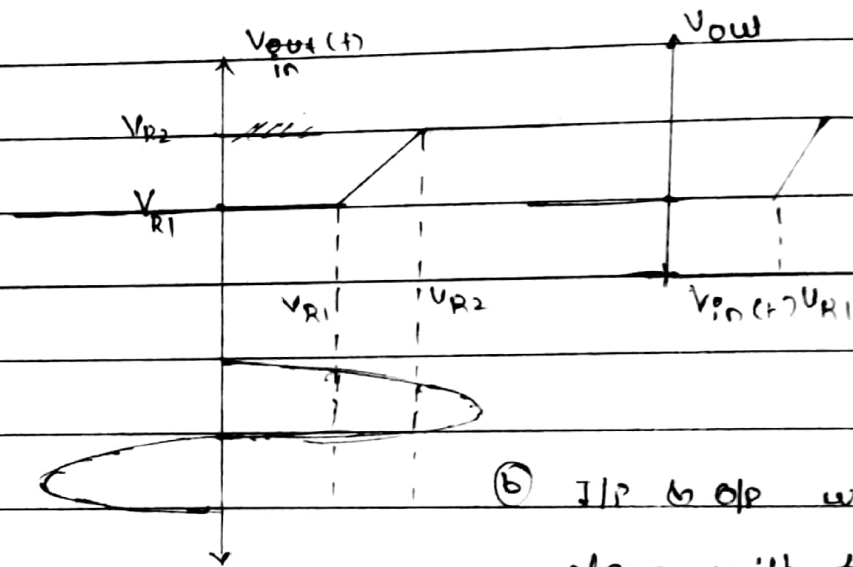

⑥ I/P & O/P waveforms along with transfer charac curve


| i/p condition              | $V_o(t)$       | Diode condition.                      |
|----------------------------|----------------|---------------------------------------|
| 1) when $V_m < V_{R1}$     | $V_o = V_{R1}$ | $D_1 = \text{ON} ; D_2 = \text{off}$  |
| 2) $V_{R1} < V_m < V_{R2}$ | $V_o = V_m(t)$ | $D_1 = \text{off} ; D_2 = \text{off}$ |
| 3) $V_m > V_{R2}$          | $V_o = V_{R2}$ | $D_1 = \text{off} ; D_2 = \text{ON}$  |

# numericals on clipping circuit.


1.

For the following diode clipping circuit, draw i/p & o/p waveforms for.

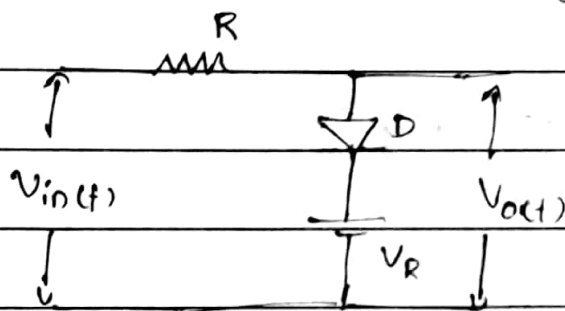a)  $R = 100\Omega$ , b)  $R = 1k\Omega$  c)  $R = 10k\Omega$  for  $V_i = 20\sin\omega t$ ,  $V_R = 10V$ ,  $R_f = 100\Omega$ ,  $R_f = \infty$ ,  $V_f = 0V$ .




$$V_m = 20V, V_R = 10V.$$

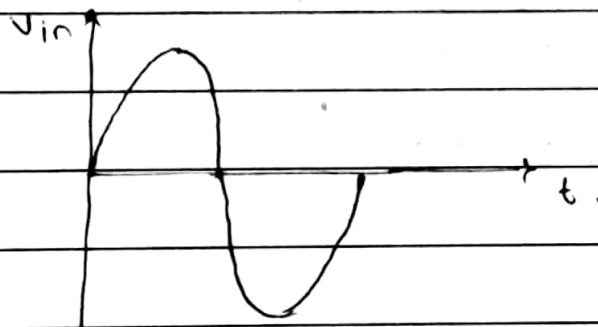

Sol: case i:  $V_m < V_R = 10V$ ;

$$V_o = V_i(t).$$

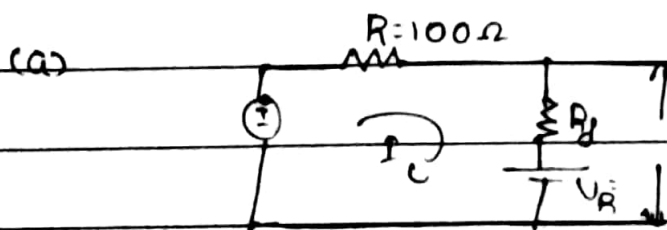case ii:  $V_m > V_R = 10V$ ; forward biased.



$$V_o = I = \frac{V_i(t) - V_R}{R + R_f} \quad \text{--- (1)}$$

$$V_o(t) = IR_f + V_R \quad \text{--- (2)}$$

$$(a) \quad V_o(t) = \left( \frac{V_i - V_R}{R + R_f} \right) \cdot R_f + V_R$$

$$= \left( \frac{20 - 10}{200} \right) 100 + 10$$



$$V_{oc(t)} = 15 \text{ V} //$$

$$(b) \quad V_o(t) = \frac{(20 - 10) \times 100 + 10}{1100}$$



$$= 10.9 \text{ V} //$$

$$(c) \quad V_o(t) = \frac{20 - 10}{(10000 + 100)} \times 100 + 10$$


$$= 10.0999 \text{ V} //$$

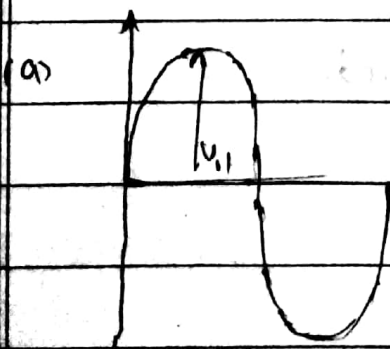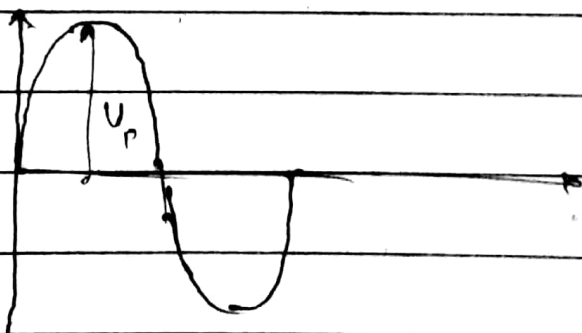



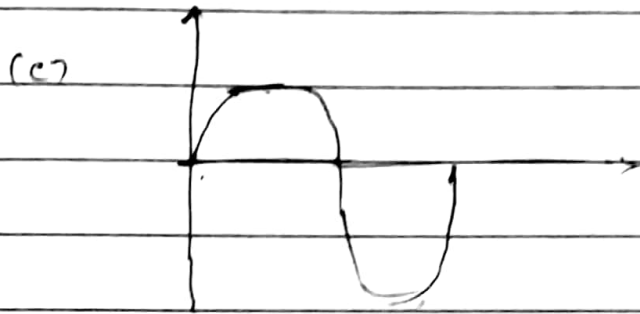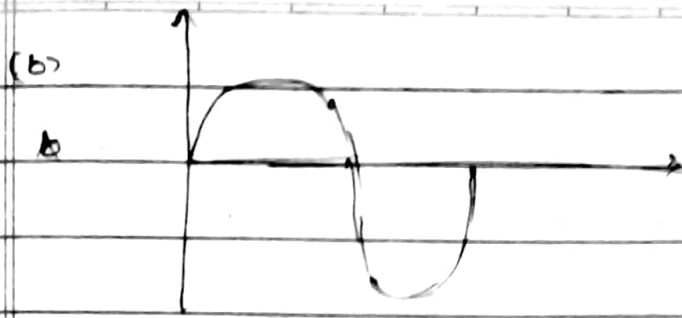


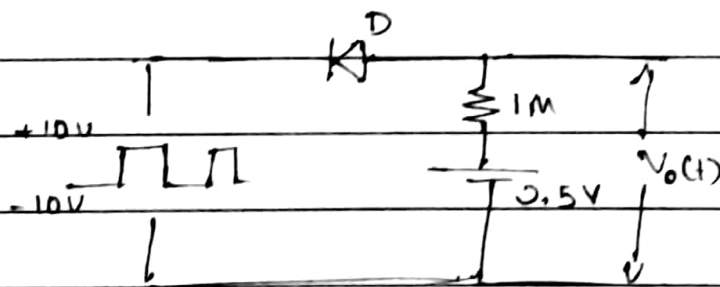2. Sketch the steady state o/p waveform for the follo. circuit indicating max., min., and constant portions assume  $R_i = 2M\Omega$ ;  $R_f = 0$ ;  $V_r = 0$ . i/p is 5kHz square wave varying bet<sup>n</sup>.  $+10V$  to  $-10V$ .



Sol<sup>n</sup>. when  $V_{in(t)} = +10V$ ;  $D$  is reverse biased and it's resist<sup>n</sup> - once  $R_i = 2M\Omega$ .

$\therefore$  The equivalent circuit is

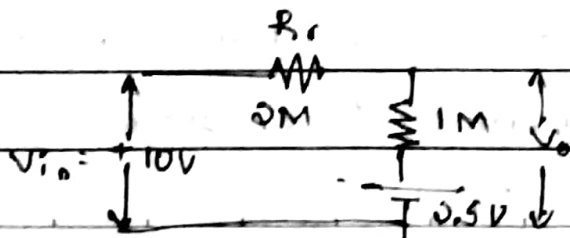



$$I = \frac{V_{in} - V_A}{R_1 + R} = \frac{10 - 0.5}{3M}$$

$$= 0.5 \mu A$$

$$\text{o/p vol } V_o = IR$$

$$= 0.5 \mu A (2.5 \times 1 \times 10^6 \times 10^{-6}) + 0.5$$

$$= 0.5 V // 5 V //$$

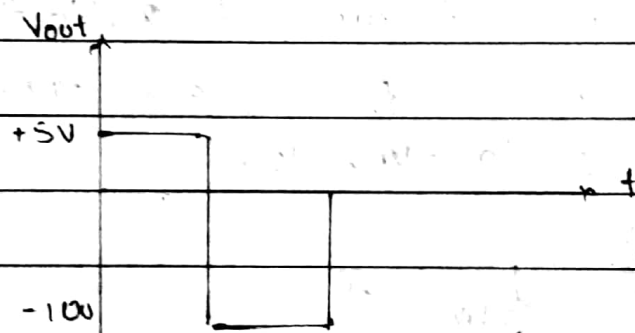
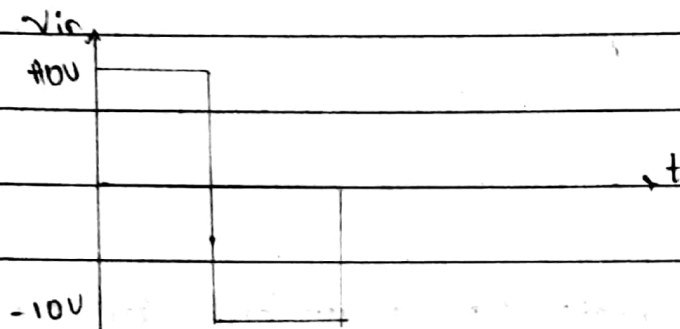


(b) when  $V_{in} = -10V$  :

D is forward biased ; It's circuit is short

$$\therefore V_o = V_{in} = -10V //$$

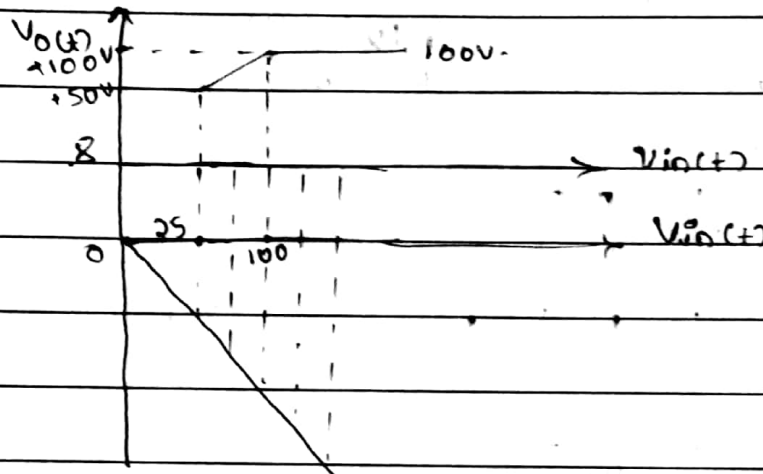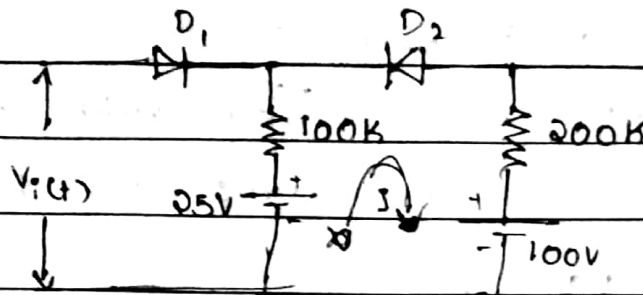3. Sketch the o/p volt. waveform over the i/p volt. for the circuit shown below given that the i/p varies linearly from 0 to 150V. assume ideal diodes.



Soln:

(i)

$$I = \frac{-100 + 25}{(200 + 100) \times 10^3}$$

when  $V_{in} < 25V$ .

$$I = -0.25 \text{ mA}$$

$$V_o = I(200 \times 10^3) + 100$$

$$= -50 + 100$$

$$= 50V //$$

(ii)

when  $V_{in} > 25V$ ,  $V_{in} < 100V$ ,  $D_1$  &  $D_2$  are forward bias.

$$V_o(t) = V_{in}(t)$$



(iii)

when  $V_{in} > 100V //$  $D_1$  is on,  $D_2$  is off.

$$\therefore V_o(t) = 100V //$$

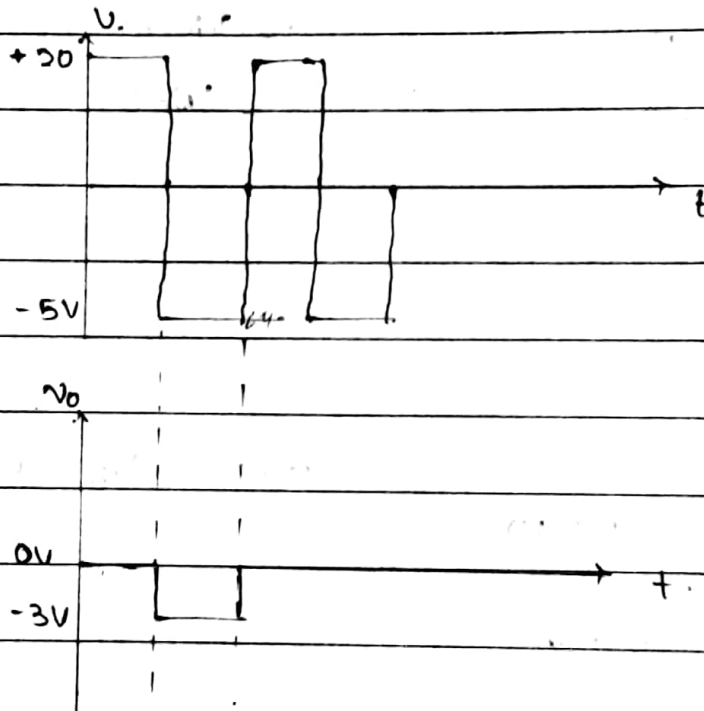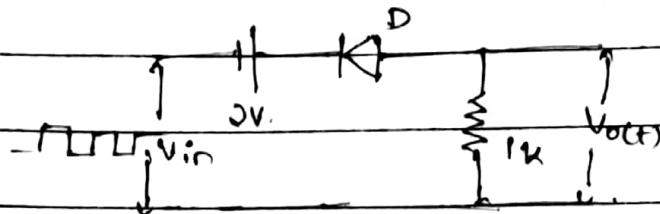
4).


The i/p to the follo. circuit is square wave making excursion betn  $+20V$  &  $-5V$  with equal +ve & -ve intervals plot o/p waveform assume ideal diode.



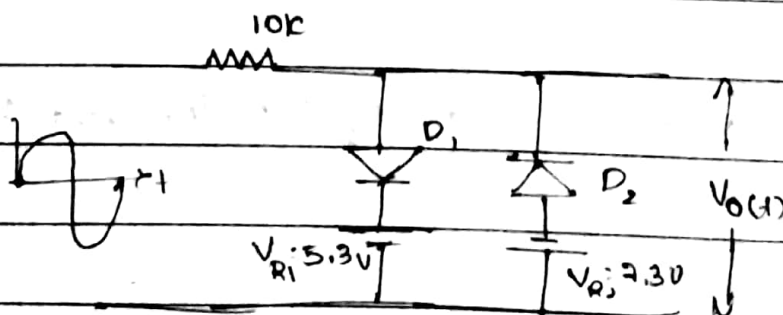
5).

Draw the o/p waveform for the follo. circuit assume  $R_f = 0$ ,  $R_s = \infty$ ,  $V_D = 0.7V$



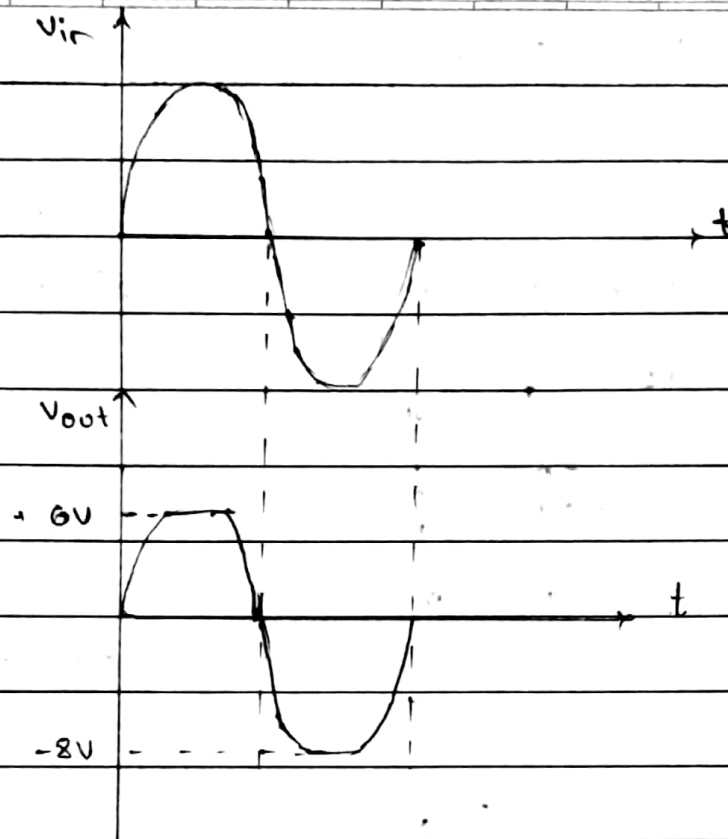

Sol<sup>n</sup>: Eq circuit.

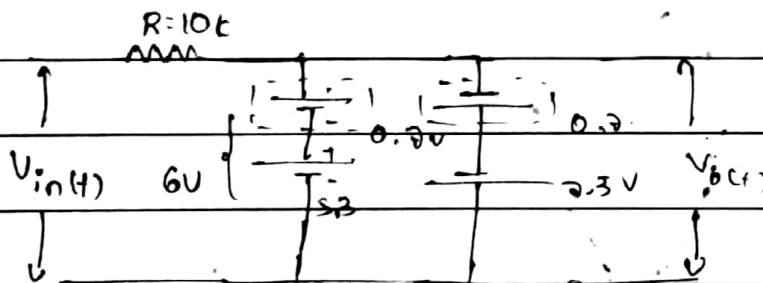

when  $V_{in} \geq 6V$ .

$D_1$  is forward biased.

when  $V_{in} \leq -8V$

$D_2$  is forward biased

23/08/17

for dc -  $T(\text{time}) = \infty$

$$\beta = \frac{1}{T} = 0$$

$$X_c = \frac{1}{\omega T C} = \infty \text{ open circuit.}$$

Date : / /

Page No.:

Clamping circuits - (DC restoration or DC insertion)

Unbiased:

1) Positive clamping circuit [Ideal diode].

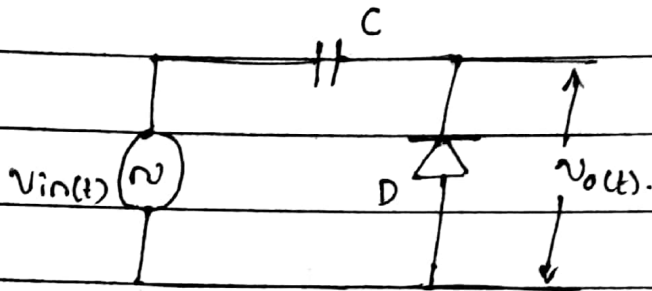


Fig 1 (a) circuit diagram



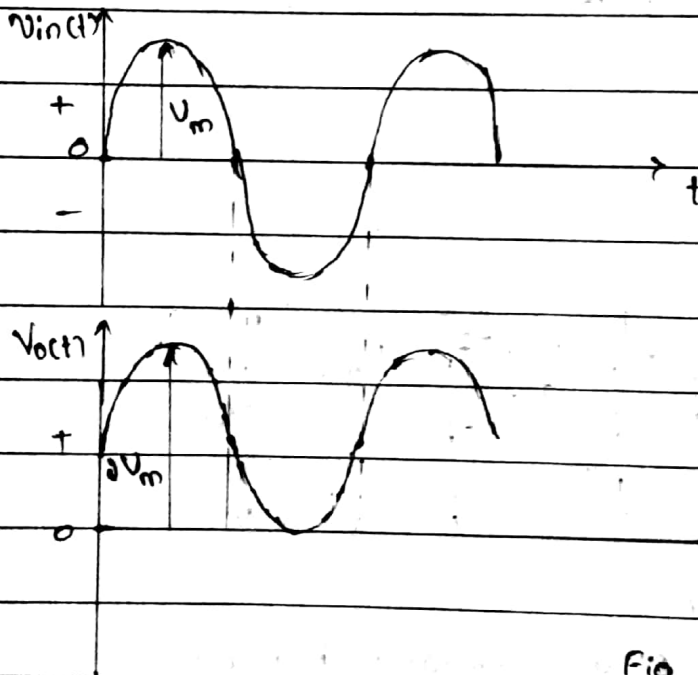



Fig 1 (b) waveforms

during -ve half cycle:


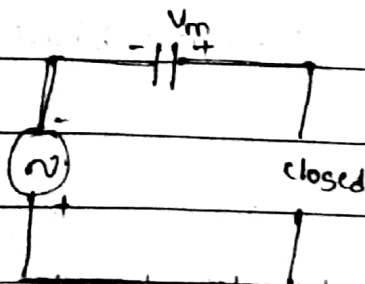


during +ve

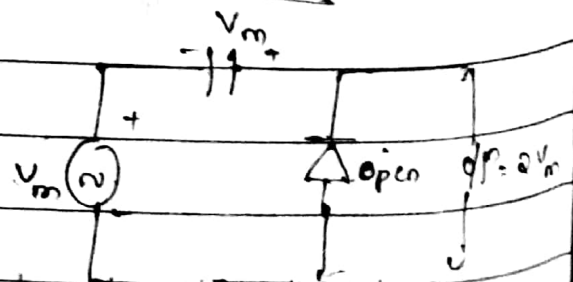

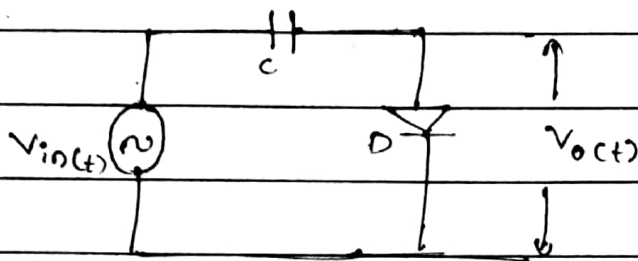
2. Negative clamping circuit


2a : circuit diagram

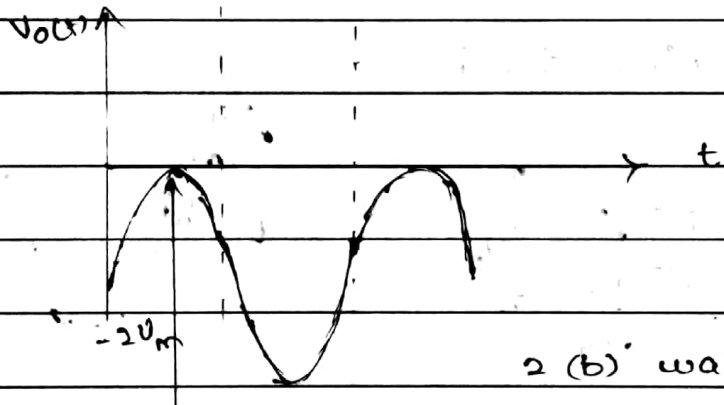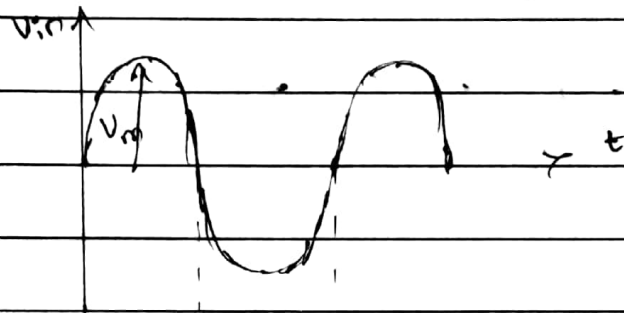



2 (b) waveform.

Ex. 2 for square wave form:

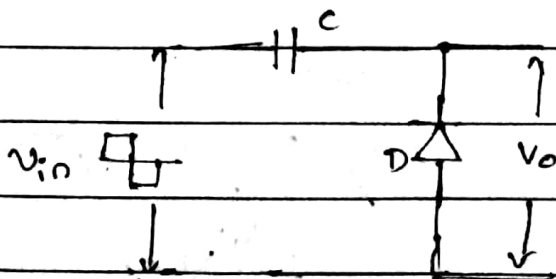


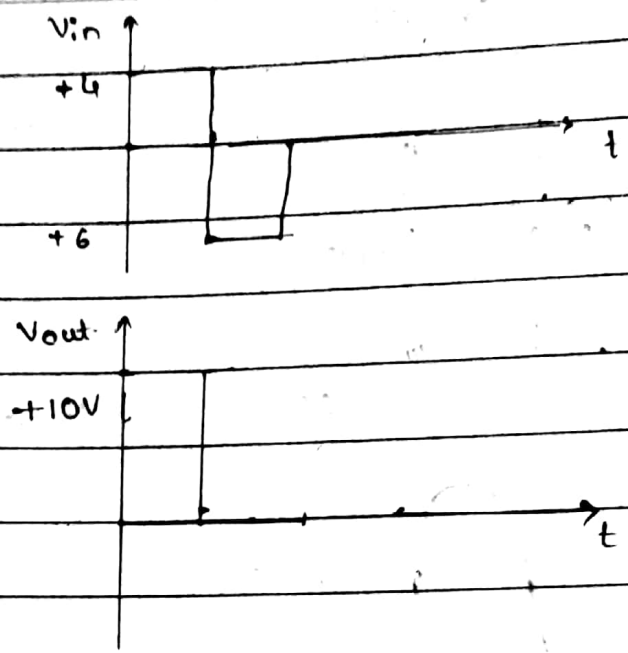

Determine  
Biased clamping circuit



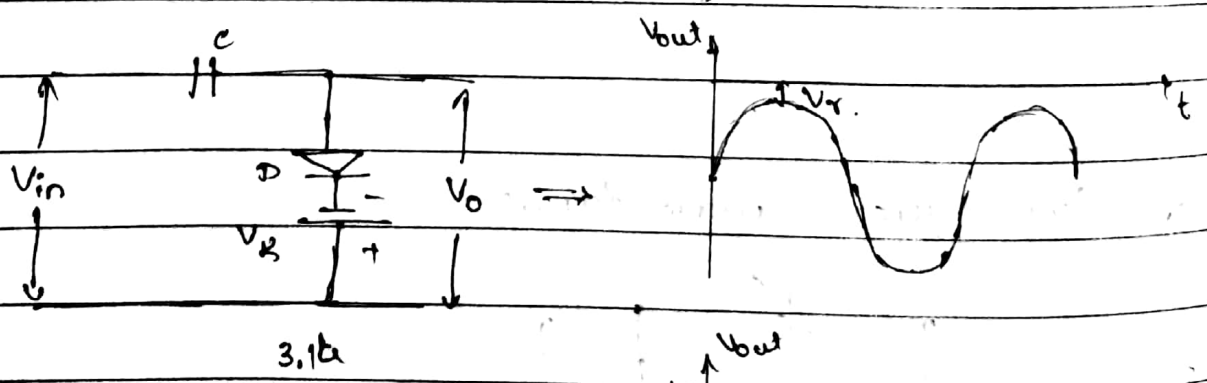
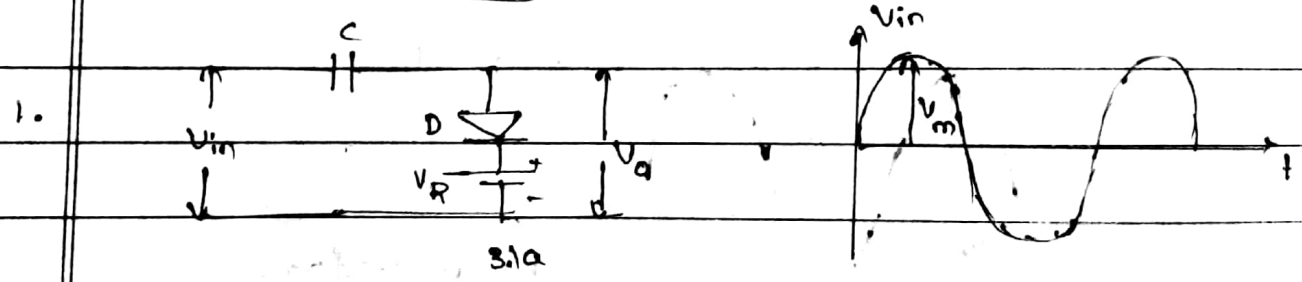


(negative)

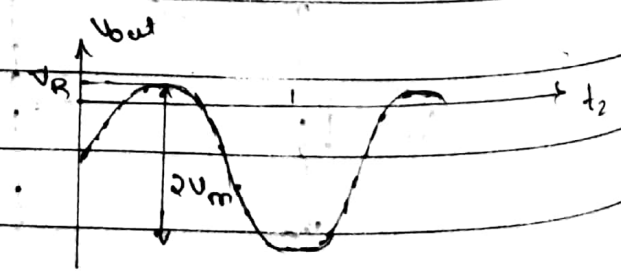



2) Positive clamping circuit.

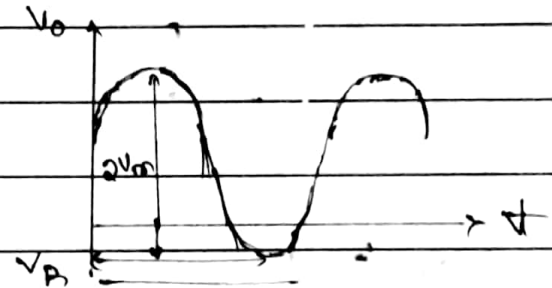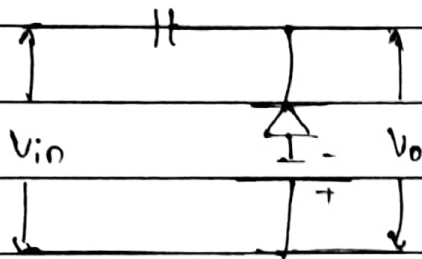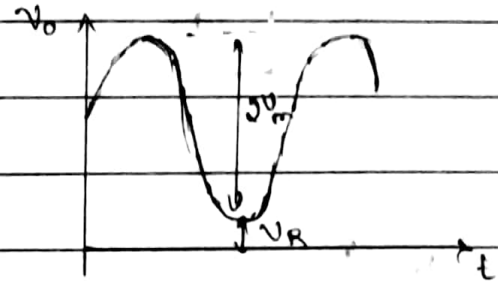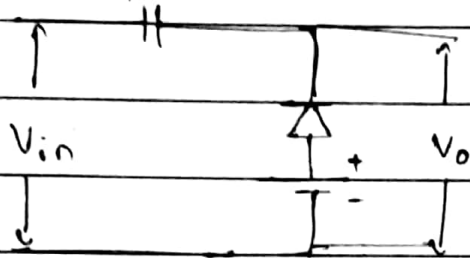


Home work:





consider square wave as the i/p and draw the circuits.

H.W

1). Biased clamping circuit:

(i) Positive

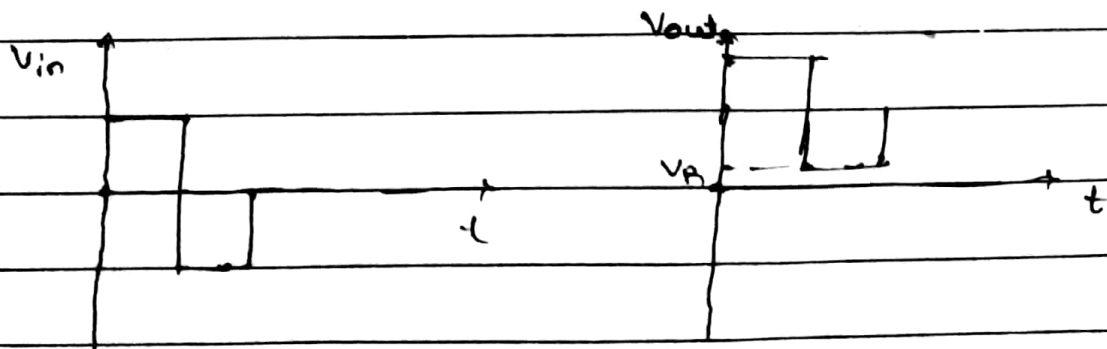

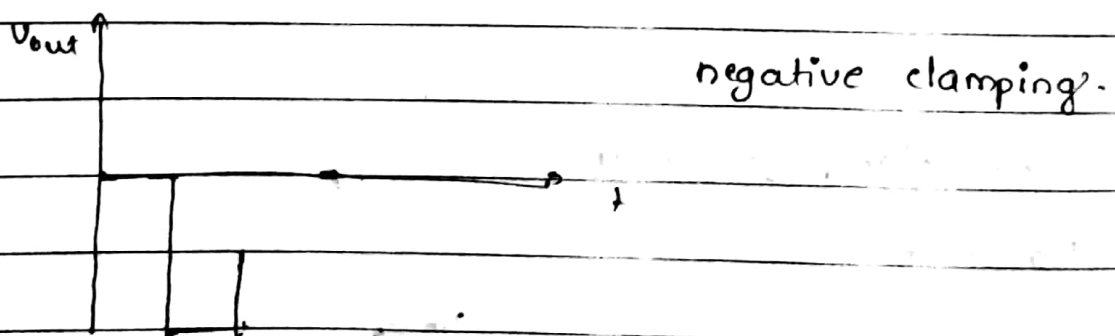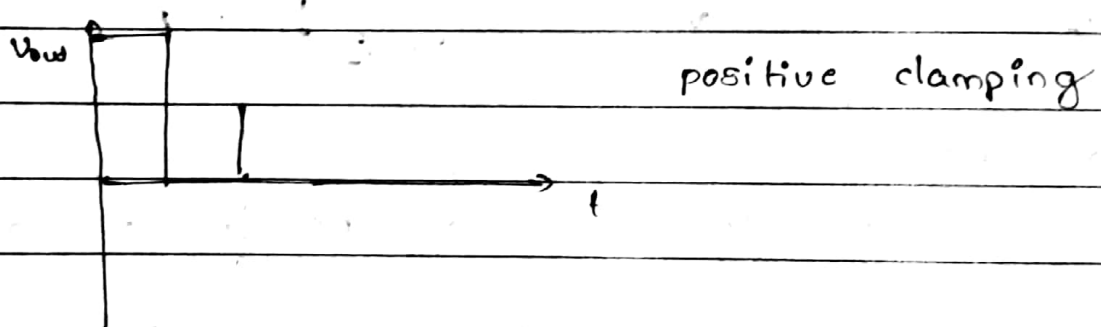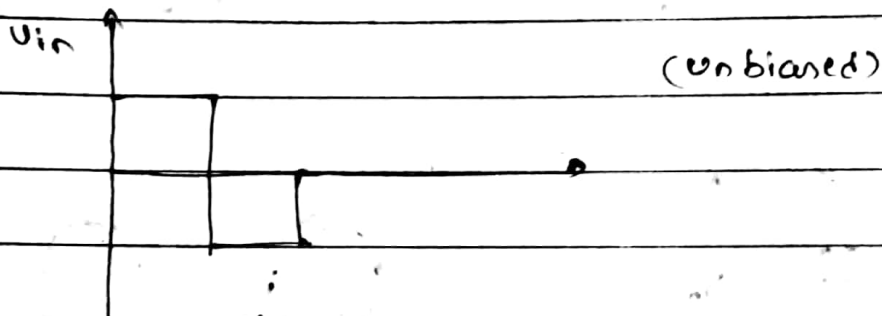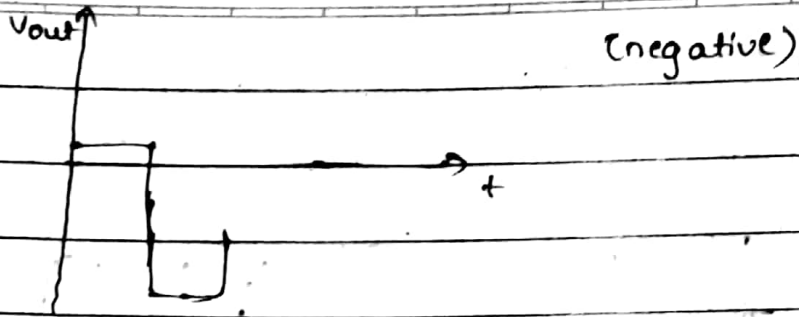


c/c = closed circuit  
o/c = open

Date: / /


Page No.:

## Problems:

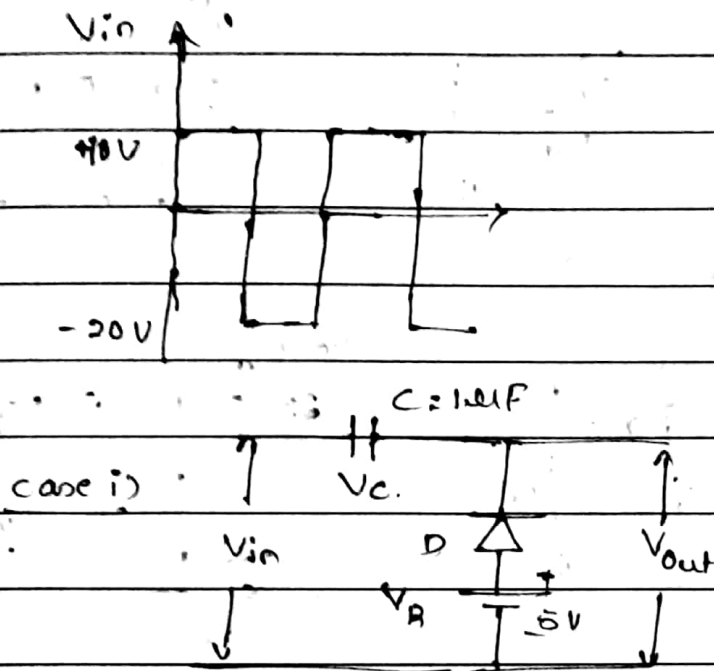
1) Determine  $V_o$  for the following circuit



Soln. during -ve half cycle.

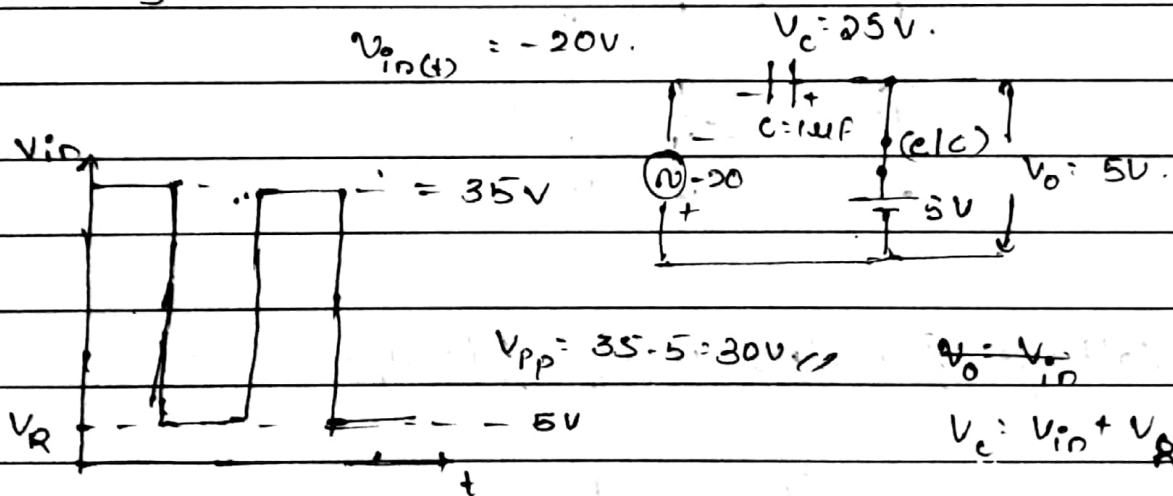


during +ve half cycle.

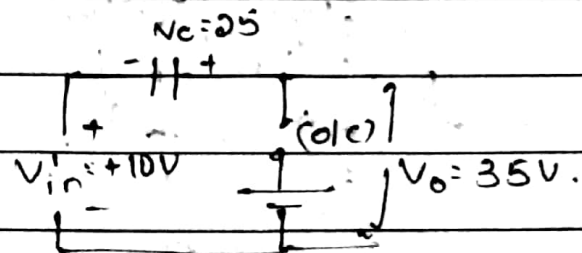


$$V_o = V_{in} + V_c = 35$$


case ii)

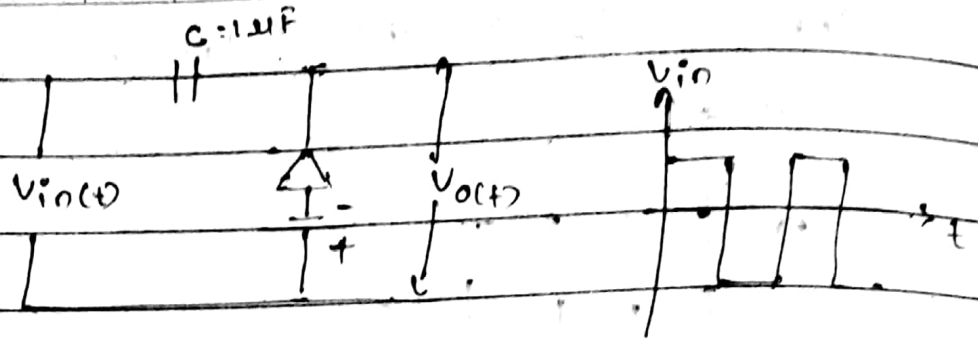


during negative half cycle

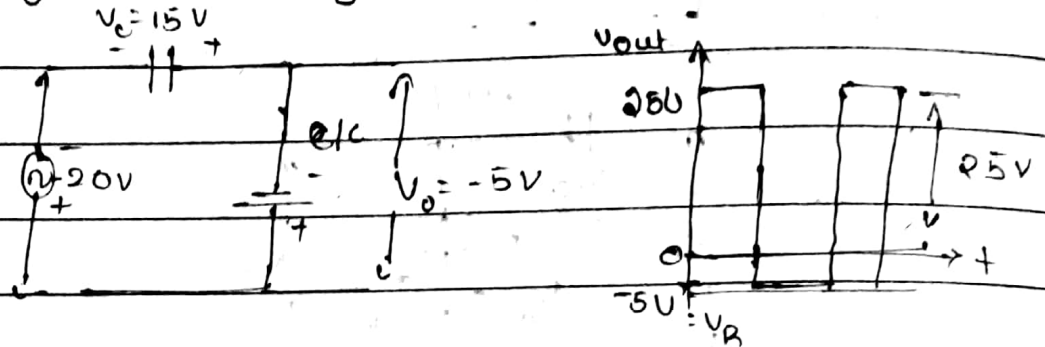


during +ve half cycle.


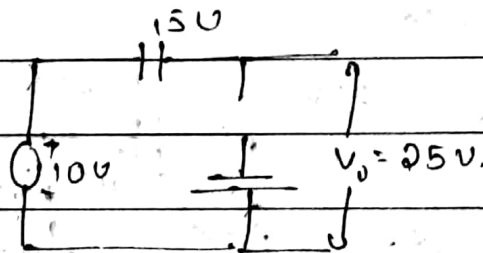
Voltage Doubler using Diodes.

(A)

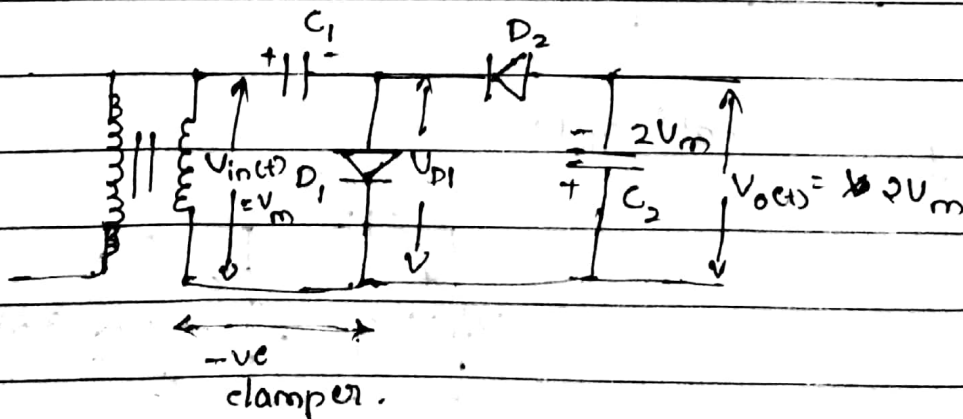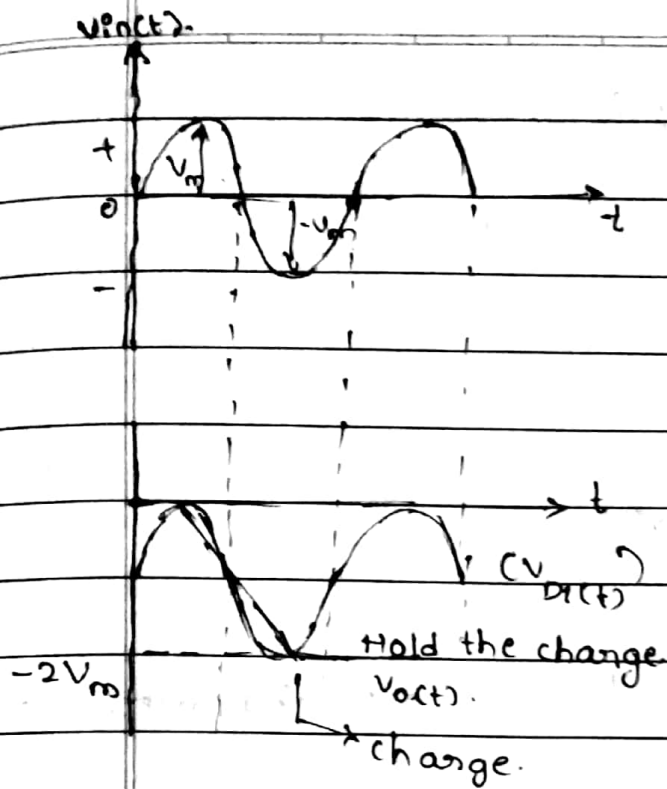Note: when  $V_{in} = V_m$ ,  $V_{out} = -2V_m$ .



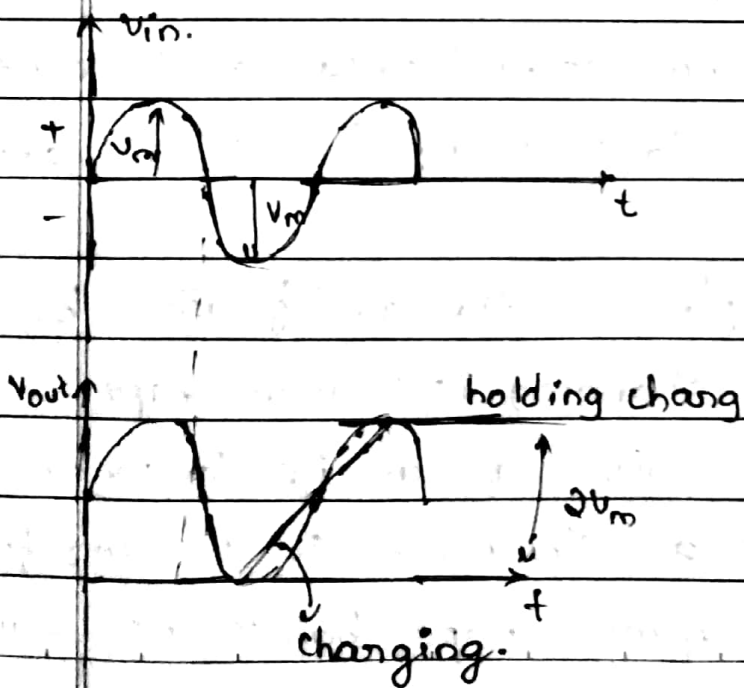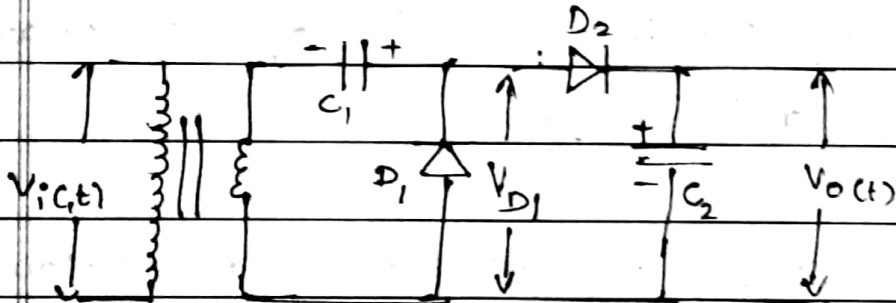B) when  $V_{in} = V_m$ ,  $V_o = 2V_m$ .




08/08/17

Date : / /

Page No.:
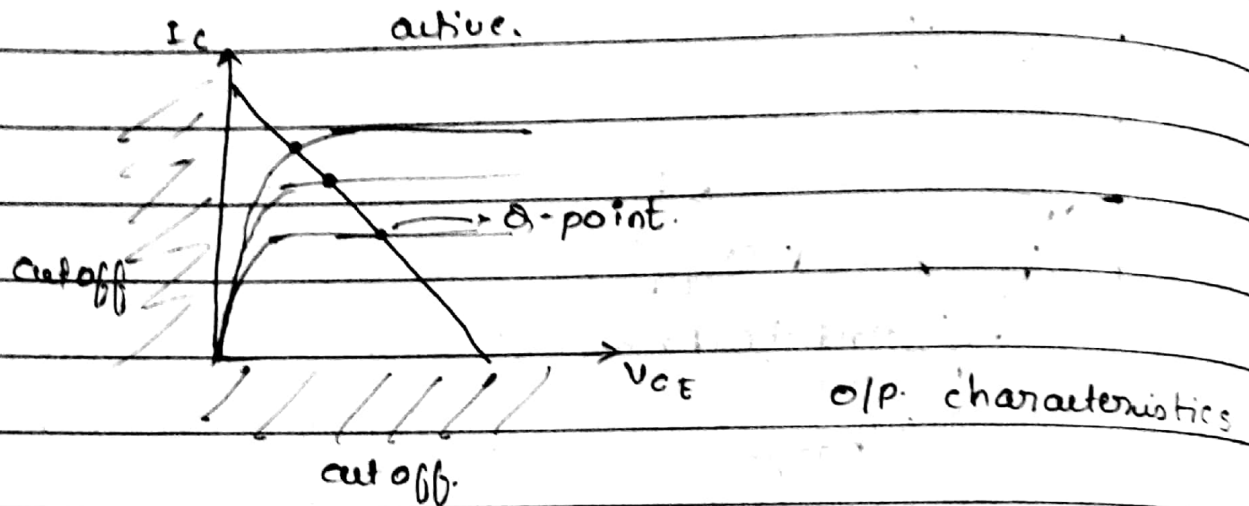
## Chapter 02 BJT Applications

Biasing  $\rightarrow$  Q-point  $\rightarrow$  Load line



Biasing is required to turn on the device so that it operates in the linear region of its charac. it is called an "active region".

Q-point or op. pt. is intersection of dc load line in the o/p char. curve

This Q-point has to be located at the centre of active region so that faithful amplification is obtained

Faithful ampl. is the amplification by an active device without changing its wave shape.

i.e. if sine wave is given as an i/p for the ampl. op should also be a sine wave in an amplified form i.e. the o/p wave shape has to be same as

the i/p.

### Biasing techniques [CE-configuration].

1. Fixed biasing or Base resistor method.
2. Emitter resistor method.
3. collector to base feedback resistor method
4. voltage divider biasing technique (Universal biasing technique).


$$I_c = \beta I_B + (1 + \beta) I_{CBO} \quad \text{--- (1)}$$

$I_{CBO} = I_{CO}$  = collector leakage current.

$$I_{CEQ} = (1 + \beta) I_{CBO} \quad \text{--- (2)}$$

★ Sequence of events occurring in a transistor which leads to thermal runaway.

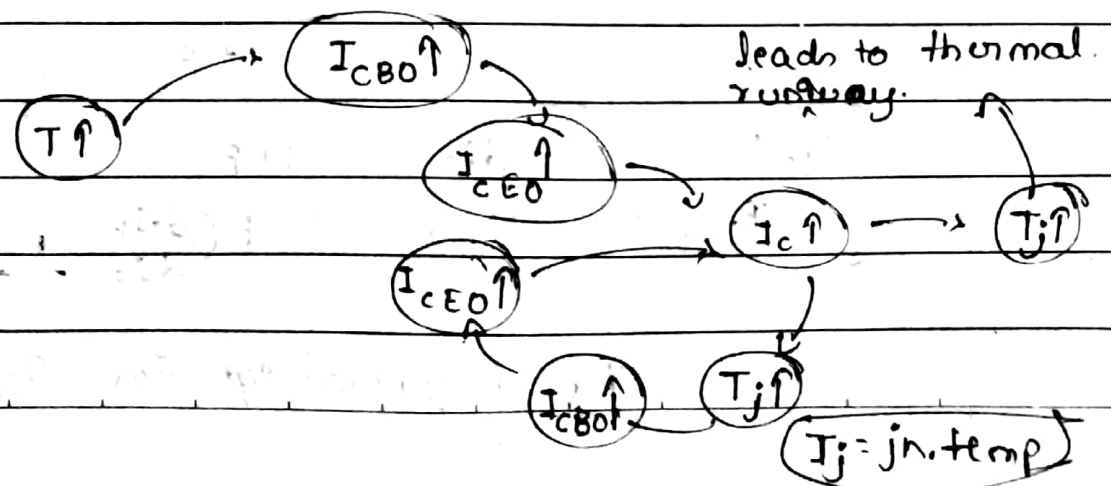Thermal runaway is self destruction of an unstabilised transistor when there is an increase in the temp.



Note: To avoid thermal runaway, diff. types of biasing are used.

### Derivation of General eqn for stability factor ( $S_{I_{C0}}$ )

$$S_{I_{C0}} \bigg|_{V_{BE}, \beta = \text{constant}} = \frac{1 + \beta}{1 - \beta \left( \frac{dI_B}{dI_C} \right)}$$

$$S_{\beta} \bigg|_{V_{BE}, I_{C0} = \text{const}} = \frac{1 + \beta}{1 - \beta \left( \frac{dI_B}{dI_C} \right)}$$

$$S_{V_{BE}} \bigg|_{I_{C0}, \beta = \text{const}} = \frac{1 + \beta}{1 - \beta \left( \frac{dI_B}{dI_C} \right)}$$

w.k.t.  $I_C = \beta \cdot I_B + (1 + \beta) I_{C0}$  — (1)

differentiating above eqn w.r.t.  $I_C$

$$\frac{dI_C}{dI_C} = \beta \frac{dI_B}{dI_C} + (1 + \beta) \frac{dI_{C0}}{dI_{C0}} \quad \text{--- (2)}$$

$$1 = \frac{dI_{C0}}{dI_C} = \frac{1 + \beta}{1 - \beta \left( \frac{dI_B}{dI_C} \right)} \quad \text{--- (3)}$$

$$\boxed{S_{I_{C0}} \bigg|_{\beta, V_{BE} = \text{const}} = \frac{dI_C}{dI_{C0}} = \frac{1 + \beta}{1 - \beta \left( \frac{dI_B}{dI_C} \right)}} \quad \text{--- (A)}$$

This is general eqn for  $S_{I_{C0}}$ .




## Voltage divider Biasing technique

1. Using approx. method. { Here, usually  $\beta = \text{unknown}$  }
2. Using accurate method.

### 1) Using approximate method:

Analysis using

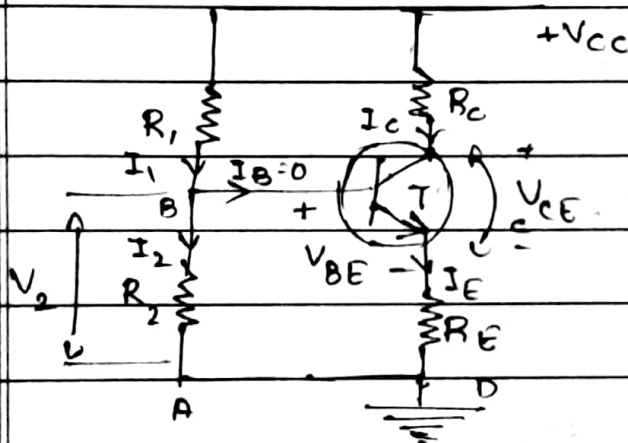

Analysis: here, Base curr.  $I_B$  is neglected for simplicity

so that  $I_E \approx I_C$  — (1)

looking at the circ. diagram we can say that

$I = I_2$  ( $I_B = 0$ ). — (2)  $\therefore$

$\therefore I = \frac{V_{CC}}{R_1 + R_2}$  — (3)

$V_2 = I R_2$  or  $I R_2$

$$V_2 = \frac{V_{CC}(R_2)}{R_1 + R_2}$$

Applying KVL to ABCDA.

$$V_D = V_{BE} + I_E R_E$$

$$= V_{BE} + I_C R_E$$


$$I_C = \frac{V_D - V_{BE}}{R_E} \quad \text{--- (7)}$$

applying KVL to o/p loop.

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E \quad \text{--- (8)}$$

$$\text{sol}^n \quad I_E = I_C$$
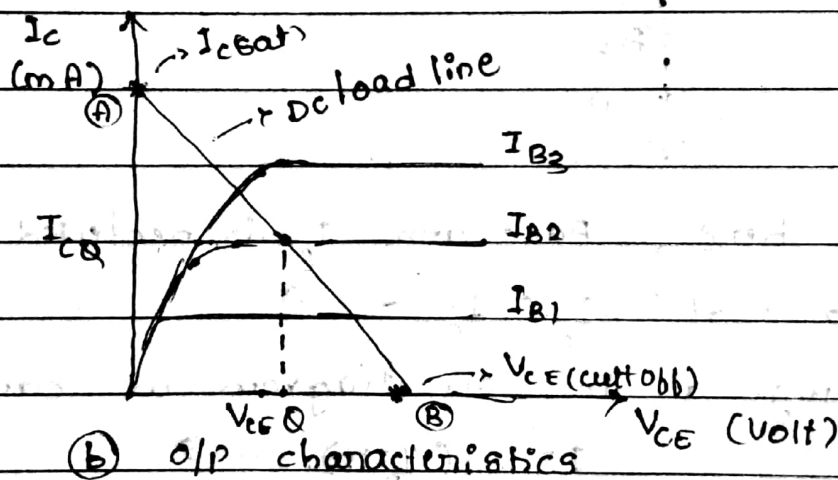
$$V_{CC} = I_C (R_C + R_E) + V_{CE} \quad \text{--- (9)}$$



consider eqn '9' and let us put  $V_{CE} = 0$

$$I_C = \frac{V_{CC}}{R_C + R_E} \quad \text{--- Pt (A)}$$

$$\text{let } I_C = 0$$

$$V_{CE} = V_{CC} \quad \text{--- pt (B)}$$

(cutoff)

DC load line

2) Analysis using accurate method.



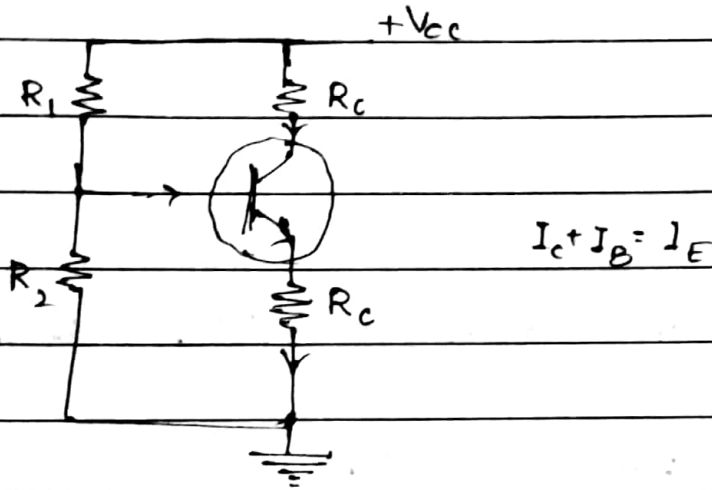
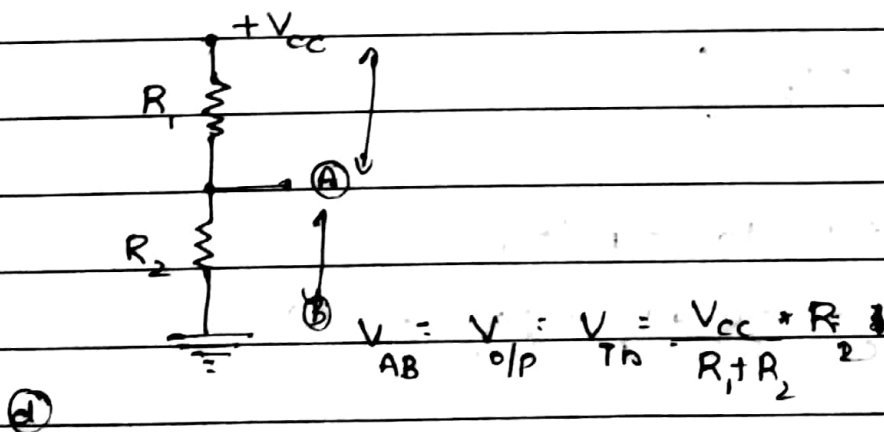


Fig 2, a

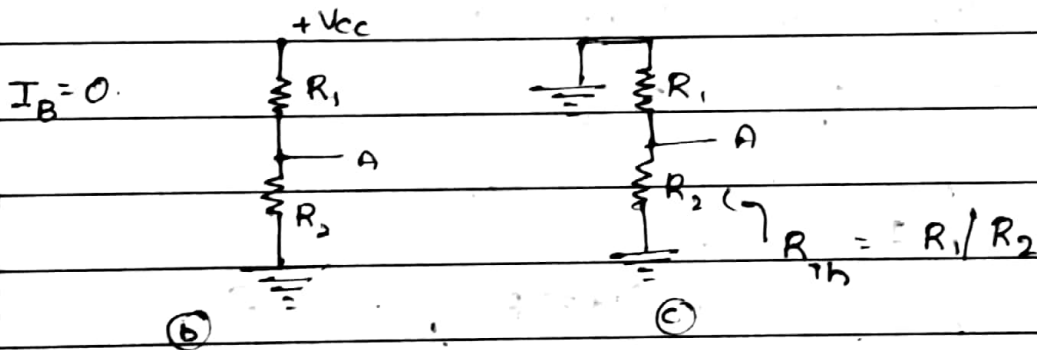

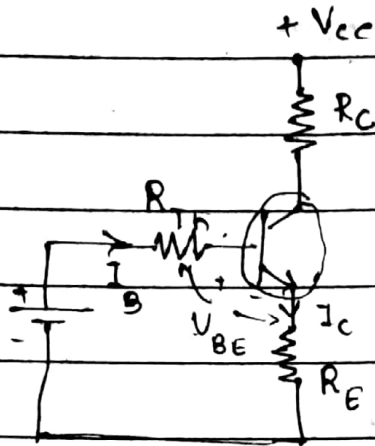

(c) Thevenin's equivalent ckt. to the i/p section

Analysis: Apply KVL to the i/p loop.

$$V_{Th} = I_B R_{Th} + V_{BE} + I_E R_E$$

$$\text{Sub: } I_E = (1 + \beta) I_B$$

$$I_B = \frac{V_{Th} - V_{BE}}{R_{Th} + (1 + \beta) R_E} \quad \text{--- (A)}$$

$$I_C = \beta I_B$$

Apply KVL to o/p loop

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E \quad \text{--- (4)}$$

neglecting  $I_B$ ,  $I_E \approx I_C$

$$V_{CC} = I_C R_C + V_{CE} + I_C R_E \quad \text{--- (5)}$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E} \quad V_{CE} = V_{CC} - I_C (R_C + R_E) \quad \text{--- (6)}$$

$\therefore Q_{pt} (V_{CEQ}, I_{CQ})$ .


considering Eqn (5) &  $V_{CC} = I_C(R_C + R_E) + V_{CE}$  — (6)

we can draw dc-load line by putting  $I_C = 0$  in the upper eqn.

$$V_{CE} = V_{CC} \xrightarrow{\text{cutoff}} \text{pt (A)}$$

Put  $V_{CE} = 0$ .
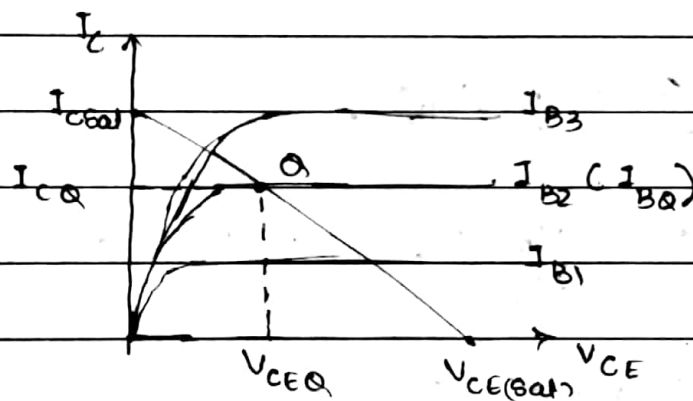
$$I_C = \frac{V_{CC}}{R_C + R_E} \xrightarrow{\text{sat}} \text{pt (B)}$$



DC load line.

Derivation of  $S_{I_{CQ}}$  for this biasing ckt.


we know that,

$$S_{I_{CQ}} / \beta \cdot V_{BE} = \frac{1 + \beta}{1 - \beta \left( \frac{dI_B}{dI_C} \right)} \quad \text{--- (A)}$$

$$S_{I_{C0}} = \frac{dI_C}{dI_{C0}}$$

Date : / /

Page No.:

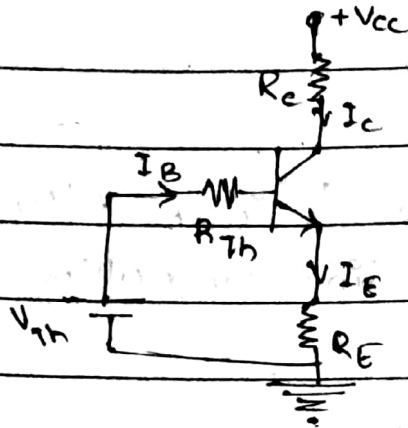

$$V_{Th} = \frac{V_{CC} \cdot R_2}{R_1 + R_2}$$

$$\therefore V_{Th} = I_B R_{Th} + V_{BE} + I_E R_E \quad \text{--- (i)}$$

$$I_{Sub} \approx I_E = I_C + I_B$$

$$V_{Th} = I_B (R_{Th} + R_E) + I_C R_E + V_{BE} \quad \text{--- (ii)}$$

$$\frac{dV_{Th}}{dI_C} = \frac{dI_B}{dI_C} (R_{Th} + R_E) + \frac{dI_C}{dI_C} R_E + \frac{dV_{BE}}{dI_C}$$

$$\frac{dV_{Th}}{dI_C} = \beta (R_{Th} + R_E)$$

$$0 = \frac{dI_B}{dI_C} (R_{Th} + R_E) + R_E + 0$$

$$\therefore \frac{dI_B}{dI_C} = -\frac{R_E}{(R_E + R_{Th})} \quad \text{--- (iii)}$$

Substituting (iii) in (A)

$$S_{I_{C0}} = \frac{1 + \beta}{1 + \beta \left( \frac{R_E}{R_E + R_{Th}} \right)}$$


In the above equation, if  $R_{Th} \ll R_E$

$$\text{then } S_{I_{C0}} = \frac{1 + \beta}{1 + \beta} = 1 //$$

To stabilise the operating point it is req. to keep the collector current variation as small as possible whenever there is leakage in.

Hence, stability factor what we obtained in this voltage biasing method is much better than any other biasing technique hence it is called as universal biasing method.

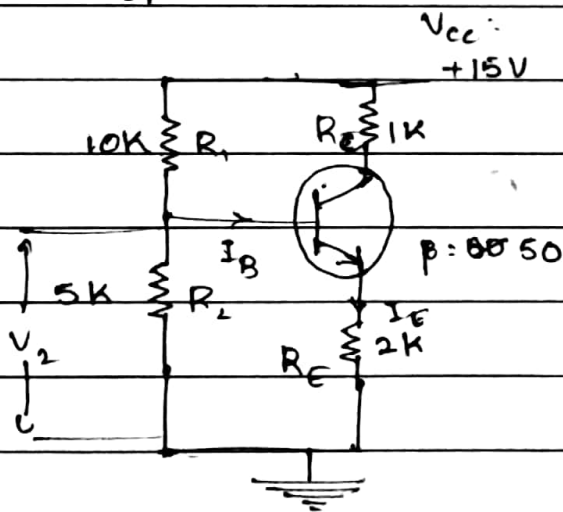- i) draw the dc load line and locate op. point for the following voltage divider biasing ckt. using approximate method as well as accurate method. transistor used is of Si type.



(a) approximate method,

$$I_1 = \frac{V_{cc}}{R_1 + R_2} = \frac{15}{10k + 5k} = 1mA$$

$$V_2 = I_1 \cdot R_2 = 1 \times 10^{-3} \times 5 \times 10^3 = 5V$$

$$V_D = I_E R_E + V_{BE} = V_{BE} + I_C R_E$$

$$I_C = \frac{V_D - V_{BE}}{R_E} = \frac{5 - 0.7}{2k} = \frac{4.3}{2k}$$

$$I_C = 2.15 \text{ mA}$$

o/p loop:

$$V_{CC} = I_C (R_C + R_E) + V_{CE}$$

$$V_{CE} = 15 - (2.15 \times 10^{-3}) (2 + 1) \times 10^3$$

$$= 15 - 6.45$$

$$V_{CE} = 8.55 \text{ V}$$

$$V_{CC} = I_C (R_C + R_E) + V_{CE}$$

put  $I_C = 0$ .

$$V_{CC} = V_{CE \text{ w/o load}} = 15 \text{ V.} \quad \text{--- (A)}$$


put  $V_{CE} = 0$

$$I_C = \frac{15}{3k}$$

$$I_{C \text{ sat}} = 5 \text{ mA} \quad \text{--- (B)}$$

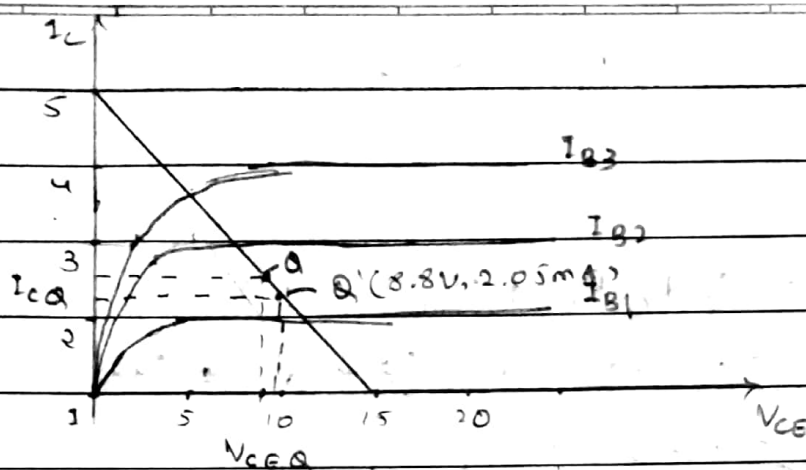
$$\therefore \text{Q-point values are } V_{CEQ} = 8.55 \text{ V, } I_{CQ} = 2.15 \text{ mA} //$$





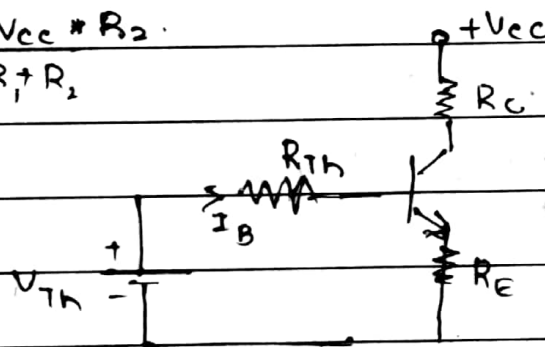b) using accurate methode.

$$V_{Th} = \frac{V_{cc} \cdot R_2}{R_1 + R_2}$$



$$V_{Th} = \frac{15 \times 5 \times 10^3}{15 \times 10^3}$$

$$R_1 = 10k = 10 \times 10^3$$

$$R_2 = 5k = 5 \times 10^3$$

$$R_1 || R_2 = \frac{10 \times 5}{15} = 3.33k\Omega$$

$$= 5V //$$

$$V_{Th} = I_{BTh} R_{Th} + V_{BE} + (1 + \beta) I_{BTh} R_E$$

$$= \frac{R_1 \times R_2}{R_1 + R_2}$$

$$V_{Th} = I_{BTh} R_{Th} + V_{BE} + (1 + \beta) I_{BTh} R_E$$

$$I_{BQ} = \frac{V_{Th} - V_{BE}}{R_{Th} + (1 + \beta) R_E}$$

$$= \frac{5 - 0.7}{(3.3 + (51)2) \times 10^3}$$

$$= 408 \mu A //$$

$$I_{CQ} = \beta I_B = 50 \times 40.8 \mu A = 2.05 \text{ mA} //$$

O/P loop

$$V_{CE} = I_C(R_C + R_E) + V_{CE} \quad \text{--- (2)}$$

$$V_{CE} = - (2.05 \times 10^{-3}) (3 \times 10^3) + (15)$$

$$V_{CEQ} = 8.85 \text{ V} //$$

$V_{CC}$  = considering (3) let us determine dc load line

pt -

$$\text{put } V_{CE} = 0, I_C = 0$$

$$V_{CE} = V_{CC} = 15 \text{ V}$$

$$V_C = 0$$

$$I_{CQ} = \frac{15}{3 \times 10^3} = 5 \text{ mA}$$

Q-point values are  $V_{CEQ} = 8.85 \text{ V}$

$$I_{CQ} = 2.05 \text{ mA}$$

$$(8.8 \text{ V}, 2.05 \text{ mA}) = Q_1$$


$$S_{ICQ} = \frac{1 + 50}{1 + 50 \left( \frac{2}{5.3} \right)} = 0.56$$

31/08/2012

Date : / /

Page No.:

2).

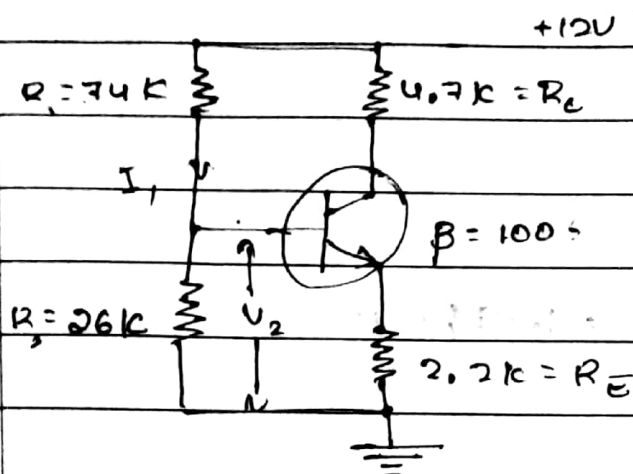

a) approx. method.

$$I_1 = \frac{V_{CC}}{R_1 + R_2} = \frac{12}{(74 + 26) \times 10^3} = 0.12 \text{ mA}$$

$$V_2 = I_1 R_2 = (0.12 \times 10^{-3}) (26 \times 10^3) = 3.12 \text{ V}$$

$$V_2 = I_E R_E + V_{BE} \quad (I_C = I_E \quad \therefore I_B = 0)$$

$$= I_C R_E + V_{BE}$$

$$I_C = \frac{3.12 - 0.7}{2.2 \times 10^3}$$

$$I_C = 1.1 \text{ mA}$$

D/P loop.

$$V_{CC} = I_C R_C + I_C R_E + V_{CE}$$

$$V_{CE} = \frac{V_{CC}}{I_C (R_C + R_E)} = \frac{12}{1.1 \times 10^{-3} (4.7 + 2.2) \times 10^3}$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E) = 4.41 \text{ V}$$

— a)


put  $V_{CE} = I_C = 0$  in (a)

$$V_{CE} = V_{CE} = 12V$$

cutoff

put  $V_{CE} = 0$  in (a)
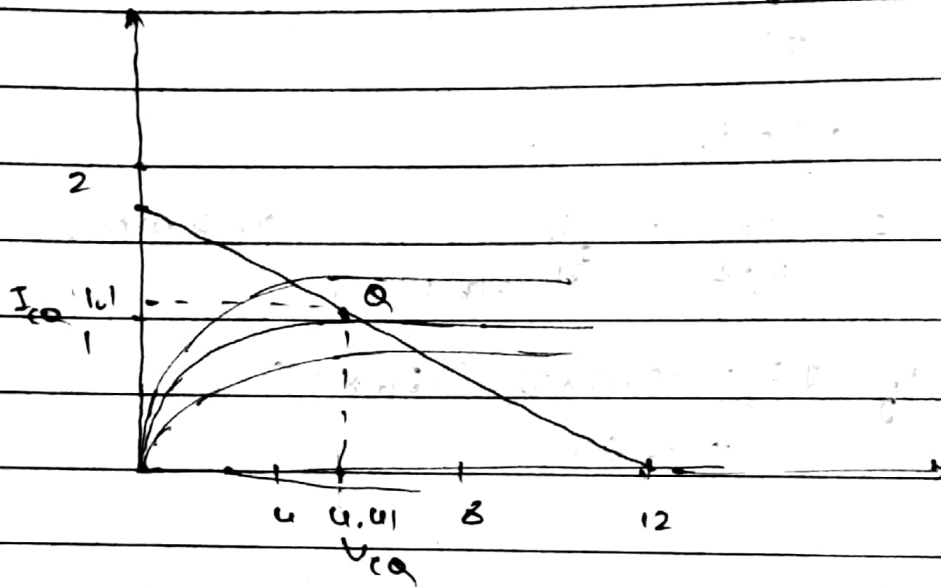
$$I_C = \frac{12}{6.9 \times 10^3} = 1.739 \text{ mA}$$



accurate method.

$$V_{TH} = \frac{V_{CC} * R_2}{R_1 + R_2} = \frac{12 * (26 \times 10^3)}{(100 \times 10^3)} = 3.12V //$$


$$R_{TH} = \frac{R_1 * R_2}{R_1 + R_2} = \frac{63 \times 26 * 34 \times 26 \times 10^6}{100 \times 10^3} = 19.24 \text{ k}\Omega //$$

Transistor modeling.

(BJT " )

re-model

hybrid model.

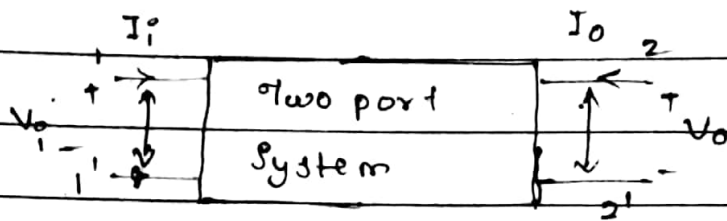Hybrid parameters & hybrid equation model for BJT

$$V_i = h_{11}I_i + h_{12}V_o$$

$$I_o = h_{21}I_i + h_{22}V_o$$

here i/p current  $I_i$  and o/p volt.  $V_o$  are consider as independent variable whereas i/p  $V_i$  and o/p current  $I_o$  are consider as dependent variable.

as  $h_{11}$  to  $h_{12}$ ,  $h_{21}$ ,  $h_{22}$  are called as hyd. hybrid parameters or. h-parameter.

$$* \left. h_{11} \right|_{V_o=0} = \frac{V_i}{I_i} = h_i = \text{short circuit i/p impedance or resistance} \Rightarrow h_{ie} \text{ (CE-conf)}$$

$$* \left. h_{12} \right|_{I_i=0} = \frac{V_i}{V_o} = h_r = \text{open ckt. reverse volt. transfer ratio.} \Rightarrow h_{re} \text{ (CE-conf)}$$

$$Z \rightarrow R - jX$$

impedance  $\rightarrow$  admittance  
reactance  $\rightarrow$  susceptance


Date: / /

Page No.:

$$* h_{21} \Big|_{V_o=0} = \frac{I_o}{I_i} = \text{short ckt forward current transfer ratio} = h_f = h_{fe} \text{ (CE)}$$

$$* h_{22} \Big|_{I_i=0} = \frac{I_o}{V_o} = \text{open ckt. conductance \& admittance} = h_o \Rightarrow h_{oe} \text{ (CE)}$$

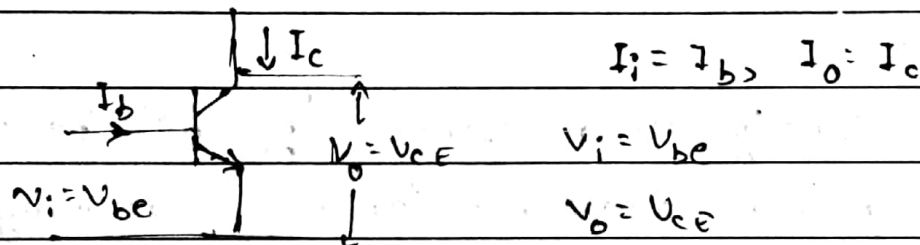
Let us use these hybrid parameters for BJT in CE configuration.



$$V_i = V_{be} = h_{ie} I_b + h_{re} V_{ce} \quad \text{--- (a)}$$

$$O, I_o = I_c = h_{fe} I_b + h_{oe} V_{ce} \quad \text{--- (b)}$$

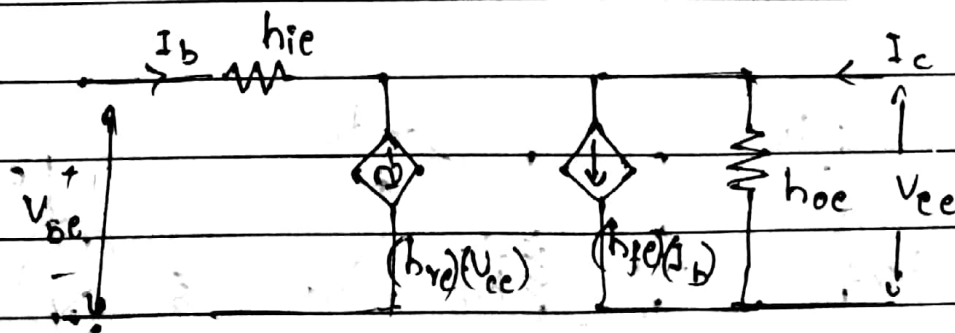considering eqs (a) & (b) let us draw equivalent ckt for BJT which is called an hybrid eq. model



Ⓑ hybrid equivalent model.

04/09/17

Date : / /

Page No.:


As seen from above hybrid model  $h_{re}$  represent reverse volt transference and this will be negligible and hence  $(h_{re} \times V_{CE})$  will be negligible. i.e.  $\{h_{re} \times V_{CE} \approx 0\}$ .

Then independent source at i/p side can be replaced by short ckt. as shown in fig.

My o/p conductance  $h_{oe}$  can also be written as  $1/h_{oe}$  by considering it as resistance then we call this circuit as an approx hybrid equivalent model.

Note:

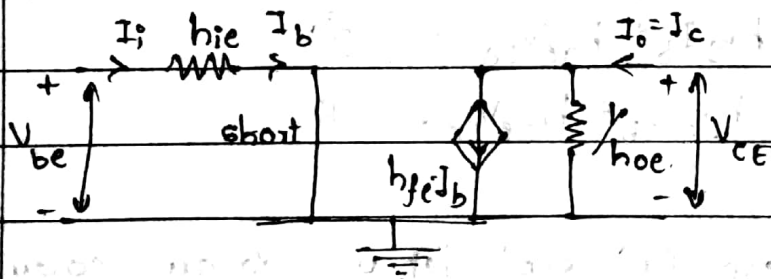Usually o/p resistance  $1/h_{oe}$  will be very large and this will be neglected for some analysis.



An approx. hybrid equivalent model fig.2

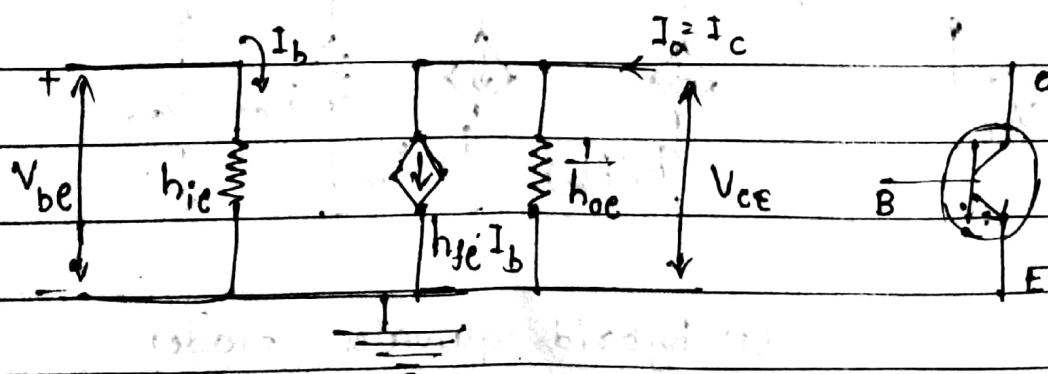


fig 2. b

Hybrid equivalent model for a voltage divider biasing network, when this is used as an amplification CE conf.

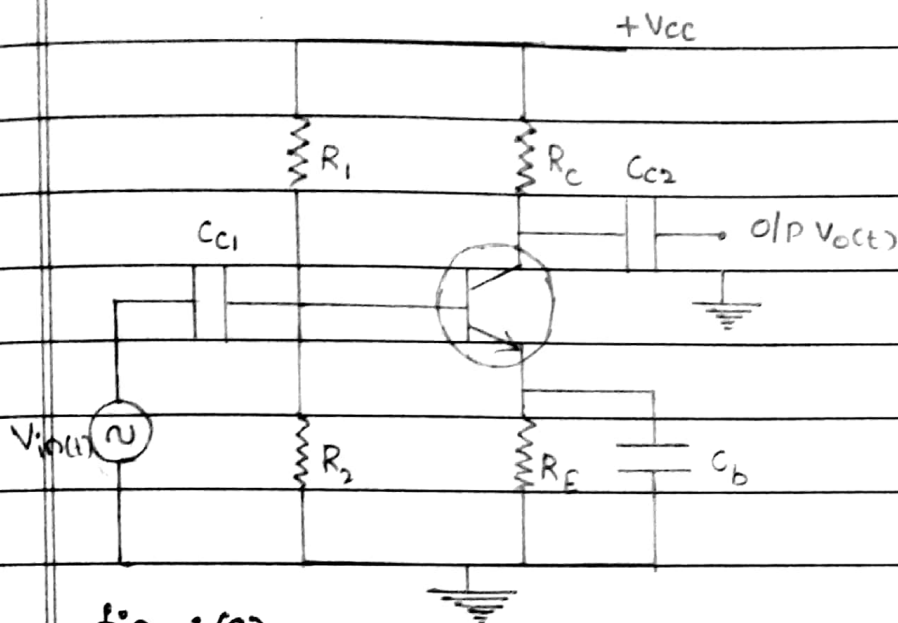


fig 1(a)


An amplifier ckt. using voltage divider biasing (CE-mode)

\*).  $C_{c1}$  &  $C_{c2} \Rightarrow$  coupling capacitor.

\*).  $C_b \Rightarrow$  By pass capacitor.

Let us draw Draw equivalent. ckt. for the ckt shown in fig (1a) this is drawn by open circuiting all the capacitors in this ckt.

1b) DC equivalent ckt.

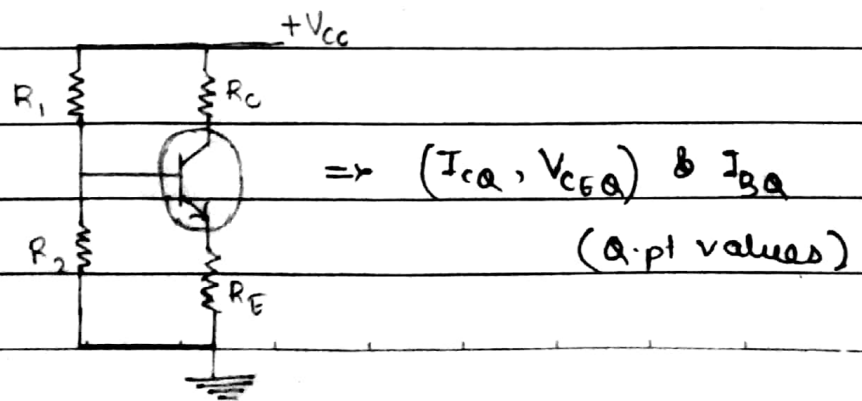



Negative sign in the above eqn shows that there is  $180^\circ$  phase difference in i/p & o/p voltages.

4). Current Gain  $A_i = \frac{I_o}{I_i}$

where  $I_i = \frac{V_i}{Z_i}$  — (a)

$I_o = V_o / Z_o$  — (b)

where  $Z_i = h_{ie} / (R_1 \parallel R_2)$  — (c)

&  $V_i = I_b \cdot h_{ie}$  — (d)

&  $Z_o = R_c \parallel (1/h_{oe})$  — (e)

$$\frac{I_o}{I_i} = \frac{V_o / Z_o}{V_i / Z_i} = \frac{V_o / [R_c \parallel (1/h_{oe})]}{V_i / [h_{ie} \parallel (R_1 \parallel R_2)]} \text{ — (f)}$$

$$\therefore A_i = \frac{I_o Z_o}{I_i Z_i} = \frac{[R_c \parallel (1/h_{oe})]}{[h_{ie} \parallel (R_1 \parallel R_2)]}$$

~~$A_i = \frac{I_o}{I_i} A_v$~~

~~$I_b = \frac{V_i}{h_{ie}}$~~

~~$I_c = \frac{V_o}{(1/h_{oe})}$~~

$$\frac{I_c}{I_b} = \frac{V_o / h_{ie}}{V_i / (h_{ie})}$$

$$A_v = \frac{V_o}{V_i} = \frac{I_c}{I_b} \cdot \frac{h_{ie}}{h_{ie}}$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{I_c}{I_b} \cdot \frac{h_{ie}}{h_{ie}} \cdot \frac{(R_c \parallel R_L)}{(R_c \parallel R_L)}$$

$$= \frac{I_c \cdot Z_o}{I_b \cdot h_{ie}} \cdot \frac{(R_c \parallel R_L)}{(R_c \parallel R_L)}$$

$$= \frac{I_c \cdot (R_c \parallel R_L)}{I_b \cdot h_{ie}} \cdot \frac{(R_c \parallel R_L)}{(R_c \parallel R_L)}$$




$$= \frac{I_c \cdot (R_c \parallel R_L)}{I_b \cdot h_{ie}} \cdot \frac{(R_c \parallel R_L)}{(R_c \parallel R_L)}$$

$$= \frac{h_{fe} \times h_{ie} \cdot (R_c \parallel R_L)}{h_{ie} (h_{ie} + R_c \parallel R_L)}$$


$$= \frac{h_{fe} \cdot (R_c \parallel R_L)}{(h_{ie} + R_c \parallel R_L)}$$

$$= \frac{h_{fe} \cdot (R_c \parallel R_L)}{(h_{ie} + R_c \parallel R_L)}$$

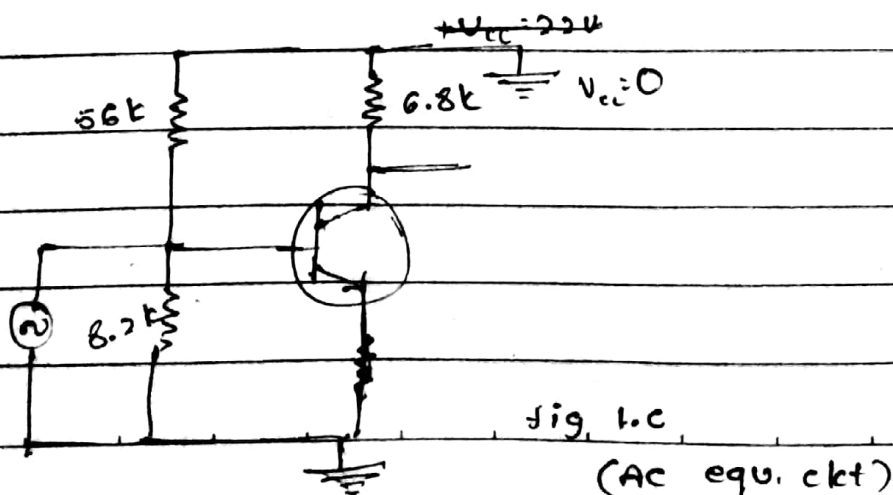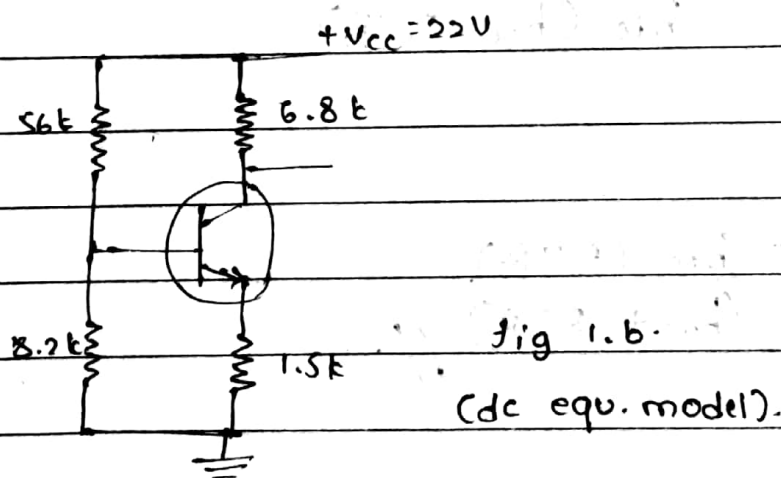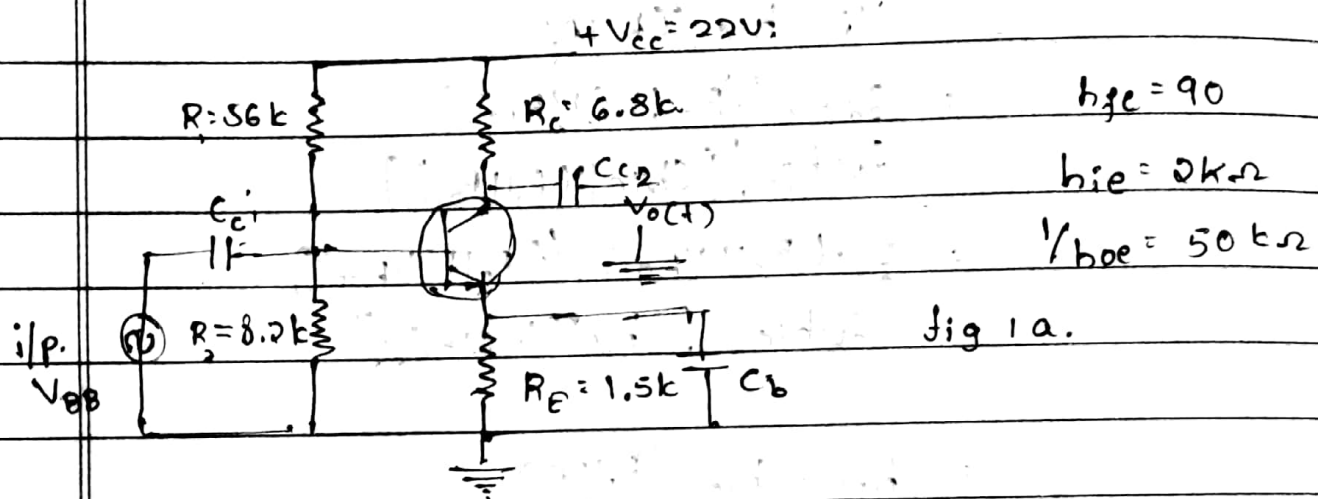- 1) Determine all four parameters of an amplifier using volt. divider ckt. given the  $R_1 = 56k\Omega$ ,  $R_2 = 8.2k\Omega$ ,  $R_C = 6.8k\Omega$ ,  $R_E = 1.5k\Omega$ ,  $V_{CC} = 22V$ . draw the ckt diagram draw its dc equ. ckt, AC equ. ckt. and corresponding hybrid model.



hybrid equivalent.

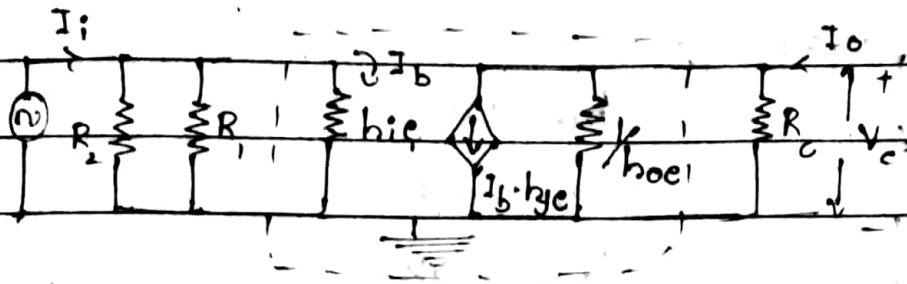


$$\begin{aligned}
 (i) \quad Z_i &= h_{ie} \parallel (R_1 \parallel R_2) \\
 &= 2000 \parallel (7.153 \times 10^3) \\
 &= 1562.98 \, \Omega \\
 \boxed{Z_i &= 1.56 \, k\Omega}
 \end{aligned}$$

$$\begin{aligned}
 (ii) \quad Z_o &= R_c \parallel 1/h_{oe} = \frac{6.8 \times 50}{(6.8 + 50)} \\
 &= 5.98 \, k\Omega
 \end{aligned}$$

$$(iii) \quad A_v = \frac{-h_{fe} (R_c \parallel 1/h_{oe})}{h_{ie}} = -269.1$$

$$(iv) \quad A_i = \frac{h_{fe} (R_1 \parallel R_2)}{[h_{ie} + (R_1 \parallel R_2)]} =$$

2).

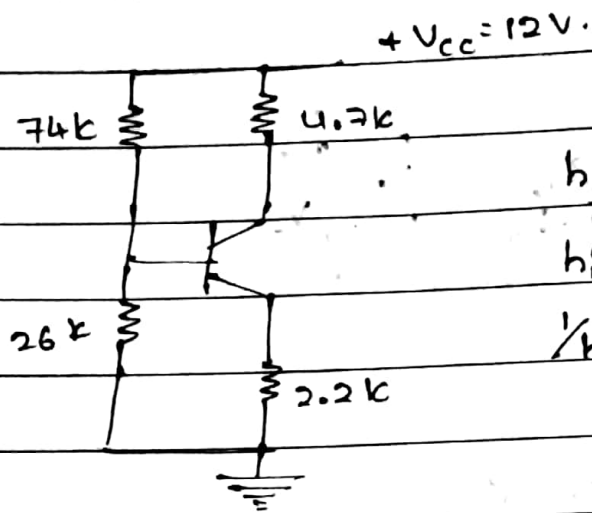

$$h_{fe} = 100$$

$$h_{ie} = 1.2k$$

$$1/h_{oe} = 50k.$$

$$i) Z_i = h_{ie} \parallel (R_1 \parallel R_2)$$

$$= (1.2 \times 10^3) \parallel \left( \frac{74 \times 26}{100} \right)$$

$$= (1.2) \parallel (19.24)$$

$$= \frac{(1.2)(19.24)}{(1.2 + 19.24)}$$

$$= 1.129 k\Omega //$$

$$ii) Z_o = R_c \parallel (1/h_{oe})$$

$$= 4.7 \parallel (50)$$

$$= \frac{(4.7)(50)}{54.7}$$

$$= 4.296 k\Omega //$$

$$\text{iii) } A_v = \frac{-h_{fe} - h_i}{h_{ie} (R_{L1} \parallel h_{oe})}$$

$$= \frac{-100 (4.296k)}{1.2k}$$


$$= -358$$

$$\text{iv) } A_i =$$

07/09/2017

Date : / /

Page No.:

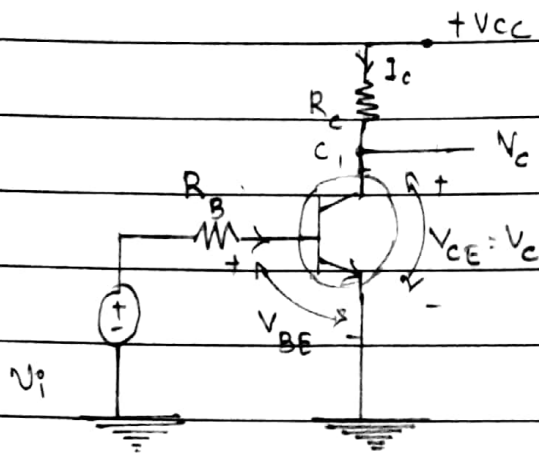BJT as a switch.

case 1:  $V_i < 0.5V, \Rightarrow I_B = 0 \Rightarrow I_C = 0 \Rightarrow$  BJT is cut off.

$$\therefore V_C = V_{CE}$$

\* Node C

case 2:

$$V_i > 0.5V.$$

now base current ( $I_B$ ) starts flowing & hence collector current  $I_C$  also starts flowing now. BJT is working in active region.

apply KVL to i/p. ckt.

$$V_i = I_B R_B + V_{BE}$$

$$I_B = \frac{V_i - V_{BE}}{R_B} \quad \text{--- (1)}$$

KVL to o/p loop.

$$I_C = \beta I_B$$

$$V_{CC} = I_C R_C + V_{CE} \quad \text{--- (2)}$$

$$\therefore V_{CE} = V_{CC} - I_C R_C \quad \text{--- (3)}$$

case 3: when i/p volt. ( $V_i$ ) is increased further so that BJT is just leaving the active region and entering into sat. region which we called as edge of saturation. (EOS)

Then, base current is denoted as  $I_{BEOS}$   
Collector current is denoted as  $I_{CEOS}$ .

KVC to o/p.

$$V_{I_{EOS}} = I_{BEOS} R_B + V_{BE} \quad \text{--- (a)}$$

then it's assume that when  $V_i$  is at EOS  $V_{CEOS} = V_C$  is taken as 0.3V. so that  $I_{CEOS}$  can be obtained using,

$$I_{CEOS} = \frac{V_{CC} - V_{CEOS}}{R_C} = \frac{V_{CC} - 0.3}{R_C} \quad \text{--- (b)}$$

case 4:

when  $V_i$  is increased further BJT enters into sat. with the increased  $I_B$  and  $I_C$  values. It should be noted that under this condition  $V_{CEsat} = V_C = 0.2V$

then  $I_{Csat}$  can be determined by:  $I_{Csat} = \frac{V_{CC} - V_{CEsat}}{R_C} \quad \text{--- (i)}$

$$= \frac{V_{CC} - 0.2}{R_C} \quad \text{--- (ii)}$$

$I_B$  value is determined using eqn  $I_B = \frac{I_{Csat}}{\beta}$

W



when BJT is operated in sat. region the actual  $\beta$  of which you can operate BJT can be easily changed to a lower value. so that we are forcing BJT to operate at lower  $\beta$  value denoted  $\beta$ -force. & what amt it has to be decreased will be decided by overdrive factor denoted as 'ODF'. this value is decided by user and this is defined as ratio of actual  $\beta$  to  $\beta$ -force

$$ODF = \frac{\beta}{\beta \text{ force}}$$

also defined as ratio of  $I_b$  to  $I_{BEOS}$

$$ODF = I_b / I_{BEOS}$$

when this ODF is given then after determining  $I_{csat}$  follo. procedure has to be followed.

v. imp when ODF is given

$$I_{csat} = \frac{V_{cc} - 0.2}{R_c} \quad \text{--- (a)}$$

$$I_{BEOS} = \frac{V_i - 0.3}{R_B} \quad \text{--- (b)}$$

$$\beta_{\text{forced}} = \frac{\beta}{ODF} \quad \text{--- (c)}$$

$$I_b = ODF \times I_{BEOS} \quad \text{--- (d)}$$


$$\text{Then } R_B = \frac{V_i - V_{BE}}{I_b} \quad \text{--- (e)}$$

Hence, BJT is operated in deep sat region. Then we call this as BJT is ON and switch is closed but switch is closed by an offset volt. of  $V_{CEsat} = 0.2V$ . i.e. actually Node 'c' should be at 0V but in actual case  $V_{CE} = V_{CEsat} = 0.2V$ .

### Problem:

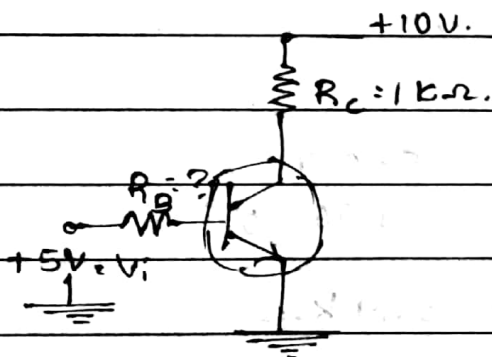- 1). The below transistor is specified to have  $\beta$  in the range of 50-150. design the value of  $R_B$  so that it operates BJT in sat. region with an ODF = 10.

Sol<sup>n</sup> Given:  $\beta = 50-150$ , ODF = 10



- Sol<sup>n</sup> a) when i/p volt  $V_i = 0V$  or say it's less than  $V_i < 0.5V$ . (Silicon).

then  $I_B = 0$ ,  $I_C = 0$ , BJT is off & switch is open.

- b) when to operate BJT in sat. so that switch is closed we have to assume  $V_{CEsat} = 0.2V$ .

$$I_{Csat} = \frac{V_{CC} - V_{CEsat}}{R_C}$$

$$I_{Csat} = \frac{10 - 0.2}{1k} = 9.8mA //$$

$$I_{BEOS} = \frac{I_{Csat}}{\beta}$$

④ It is imp. to consider min. value of  $\beta = 50$  to drive the transistor into saturation.

$$I_{BEOS} \geq \frac{9.8}{50} = 0.196mA //$$

ODF is 10

$$\therefore I_B = 10 \times 0.196mA = 1.96mA //$$

$$R_B = \frac{V_i - V_{BE}}{I_B} = \frac{5 - 0.7}{1.96 \times 10^{-3}}$$

$$= 2.19k\Omega$$

$$= 2.2k\Omega //$$

$$\beta_{force} = \frac{50}{10} = \frac{\beta}{ODF}$$

$$\boxed{\beta_{force} = 5}$$

2. Consider, the ckt of BJT as a switch. with  $V_{CC} = +5V$ ,  $V_i = +5V$ ,  $R_B = R_C = 1k\Omega$  &  $\beta = 100$  calculate the base current collector current and collector volt. if the trans. is saturated find  $\beta_{forced}$ ? what is the value of  $R_B$  to bring the trans to the edge of sat.

Soln:  $V_{CC} = +5V$ ,  $V_i = +5V$ ,  $R_B = R_C = 1k\Omega$ ,  $\beta = 100$ .

$$I_B = \frac{V_i - V_{BE}}{R_B} = \frac{5 - 0.7}{1000} = 4.3mA //$$

$$*) I_{Csat} = \frac{V_{CC} - V_{CESat}}{R_C} = \frac{5 - 0.2}{1k} = 4.8mA //$$

$$\beta_{force} = \frac{I_{Csat}}{I_B} = \frac{4.8mA}{4.3mA} = 1.12$$

$$*) ODF = \frac{\beta}{\beta_{force}} = \frac{100}{1.12} = 89.285 //$$

$$R_{BEOS} = I_{BEOS} \quad I_{CEOS} = \frac{V_{CC} - V_{CEOS}}{R_C} = \frac{5 - 0.3}{1000} = 4.7mA //$$

$$I_{BEOS} = \frac{I_{CEOS}}{\beta} = \frac{4.7mA}{100} = 0.047mA$$

$$R_{B_{cos}} = \frac{V_i - V_{BE}}{I_{BEOS}} = \frac{5 - 0.7}{0.047 \times 10^{-3}} = 91.49k\Omega$$

$$= \underline{\underline{91.5k\Omega}}$$

14/09/17

Test at

chap 03: MOSFET characteristics and its

1\*

Types of MOSFET (Metal oxide semiconductor field effect Transistor).

2 types


1) Depletion type

2) enhancement

N channel      P channel.

Constr. diagram of

NMOSFET depletion type.

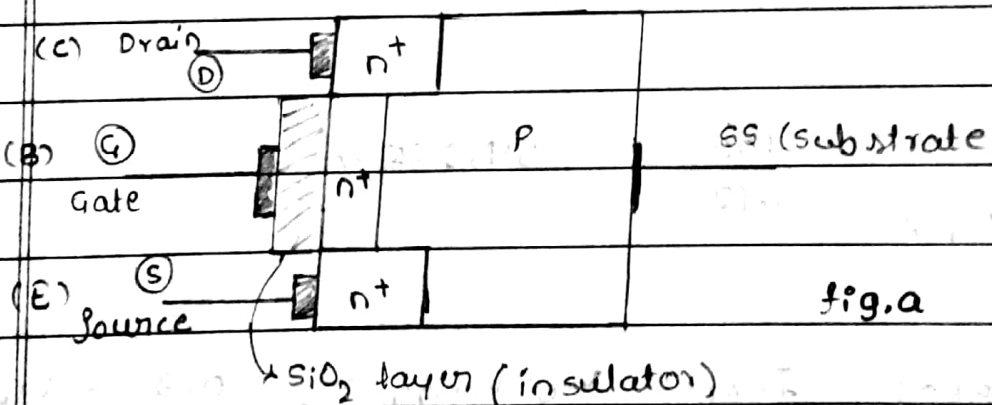

- 1> when  $V_g = 0V$
  - 2> when  $V_g = -ve$
  - 3> when  $V_g = +ve$
- }  $\rightarrow$  depletion mode.

(This part of trans char. is known as enhancement mode)

Date: / /  
Page No.:


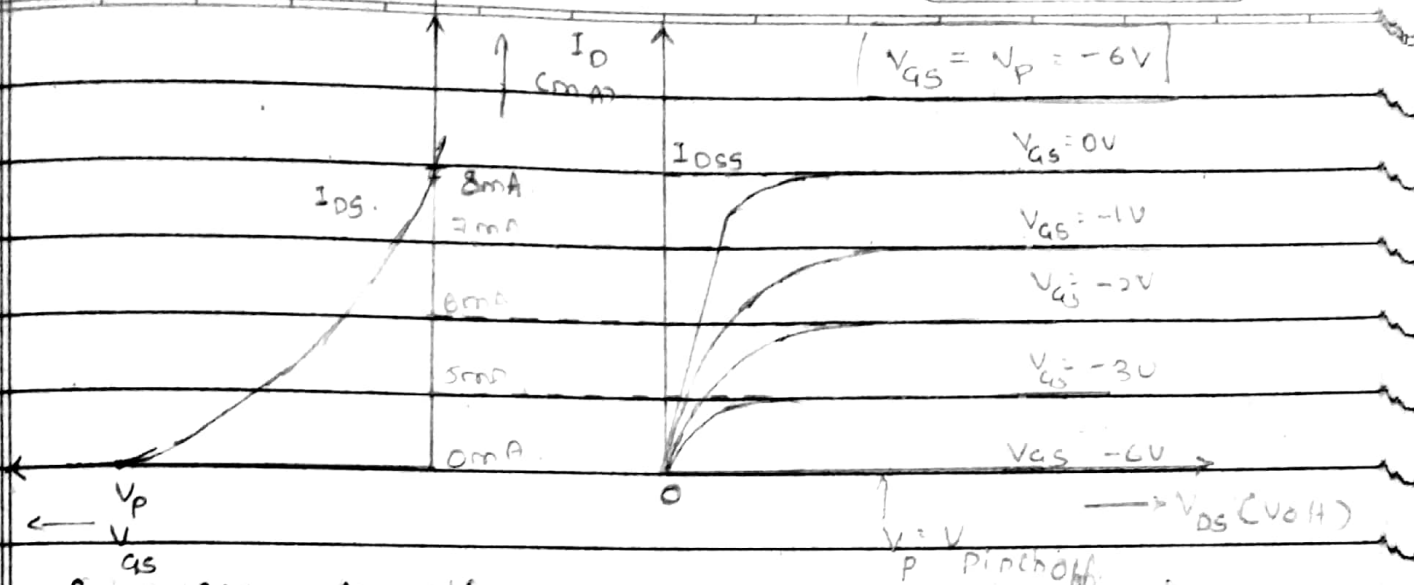



fig. b (transfer characteristics).


fig. c. (Drain / o/p. char).

N-channel.

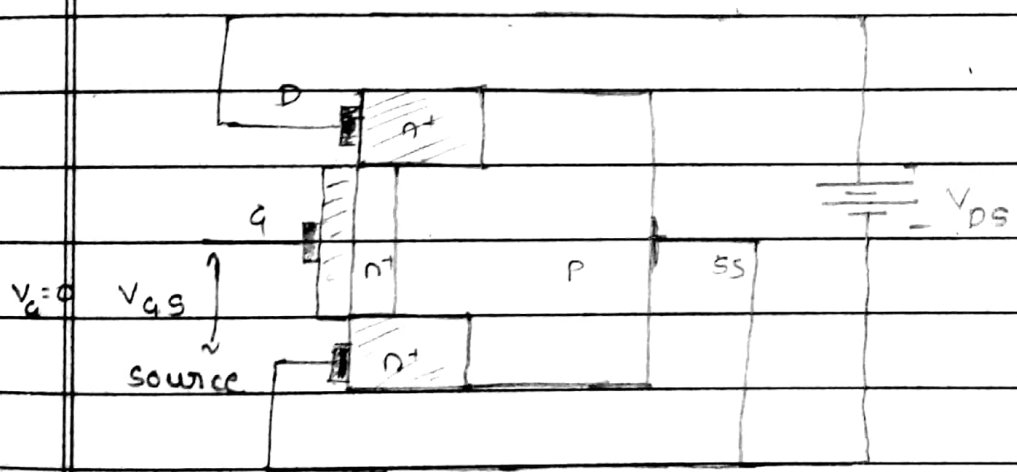

P-channel.

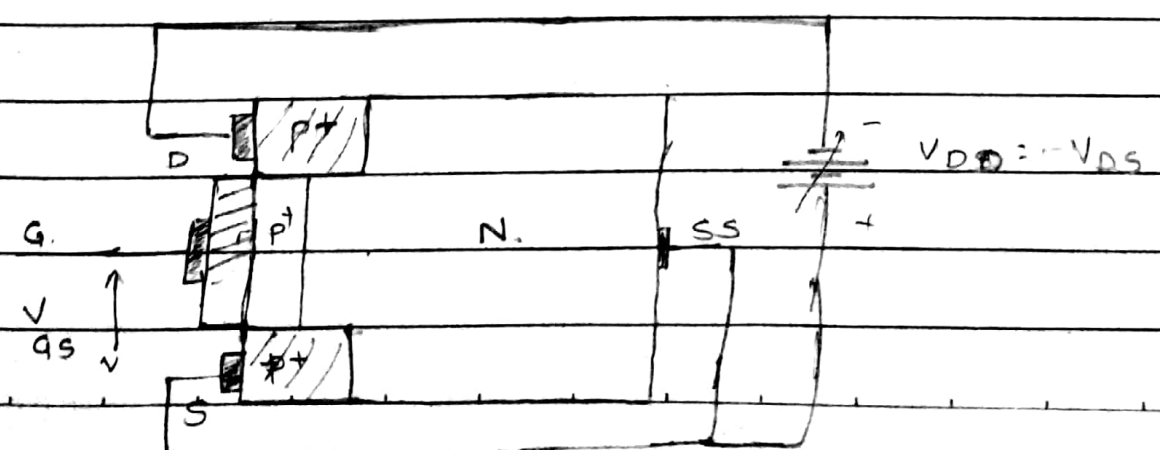

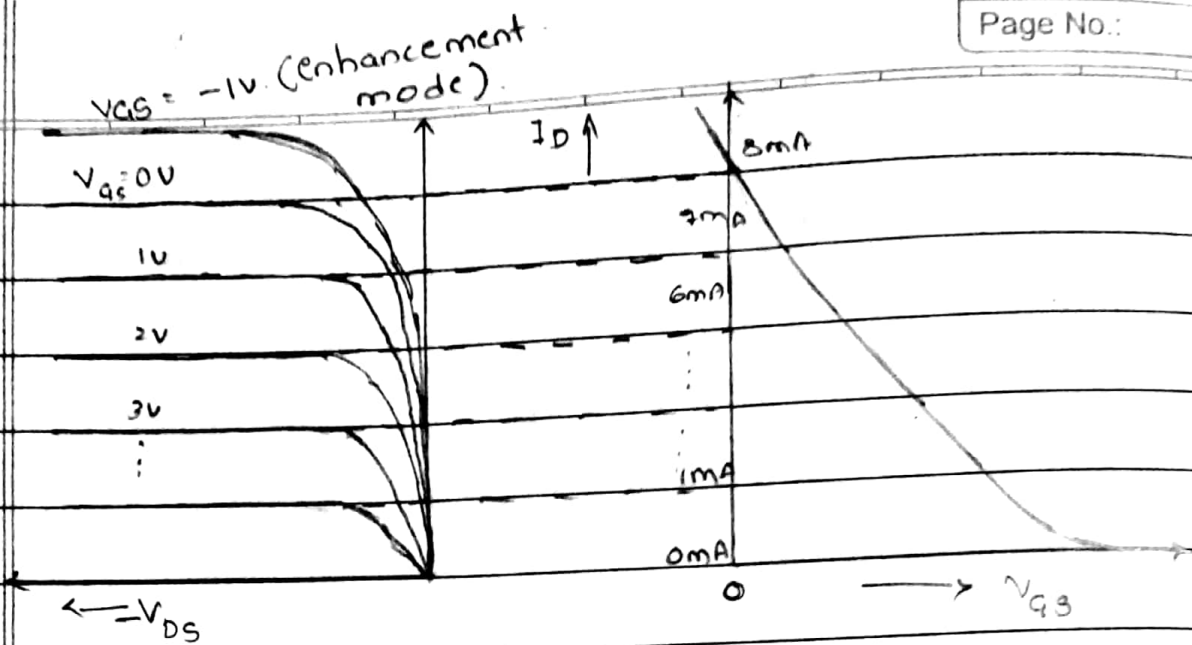

(Drain charact.)

(transfer charact.)